

~~Day 4~~

8

TUESDAY • MARCH • 2016

Paper -II

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

PN junction diode

8

By themselves P-type and N-type taken separately are of very limited use if we join a piece of P-type to a piece of N-type semiconductor such that the crystal structure remains continuous at the boundary a PN junction diode is formed, such a junction makes a very useful device called PN junction diode or simply semiconductor diode. A diode has two terminals anode and cathode, the P region is the anode and the N region the cathode, it is represented by the foll. symbol in circuits,



Sometimes you have to hold several hands when your goal is far enough.

APRIL 2016

M	T	W	T	F	S	S
1	2	3				
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	

WK 11 (069-297)

2016 • MARCH • WEDNESDAY

9

PIN junction

when there is no applied voltage or it is just formed

Consider a PN junction just immediately after it is formed, P region has holes a majority carriers while N-region has free electrons) as majority carriers, holes and free e⁻ are the mobile charges. While ions are immobile, the instant a PN junction is formed, holes and free e⁻ diffuse across the junction this is because they move randomly due to thermal energy and also due to a difference in their concentrations in the two.



S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

10

THURSDAY • MARCH • 2016

regions, therefore, near the junction, there are a large no. of free e^- and holes in both P and N type regions, therefore, there is a possibility of a free e^- combining with a hole, this combination is called recombination process. When a recombination takes place a free e^- occupies the hole and both hole and free e^- is lost due to many such recombinations close to the junction mobile carriers are lost and the overall result is that there is a positive charge on the N-side of the junction and a negative charge on the P-side, these charges are respectively due to the positive and negative ions that are immobile, the region at the junction having a depletion or absence of mobile carriers with only uncompensated positive and negative ions is called




APRIL 2016
T W T F S S
1 2 3
4 5 6 7 8 9 10
11 12 13 14 15 16 17
18 19 20 21 22 23 24
25 26 27 28 29 30

WK 11 (07/1-29/5)

2016 • MARCH • FRIDAY

11

depletion region: Once this region is formed once free e^- on the N-side cannot cross the junction because they are repelled by the uncompensated negative ions, similarly holes cannot cross-over to the N-side repelled by uncompensated positive ions thus after a few recombination in the immediate neighbourhood of the junction a barrier is set-up, this barrier prevents further diffusion of holes and free e^- across the junction.

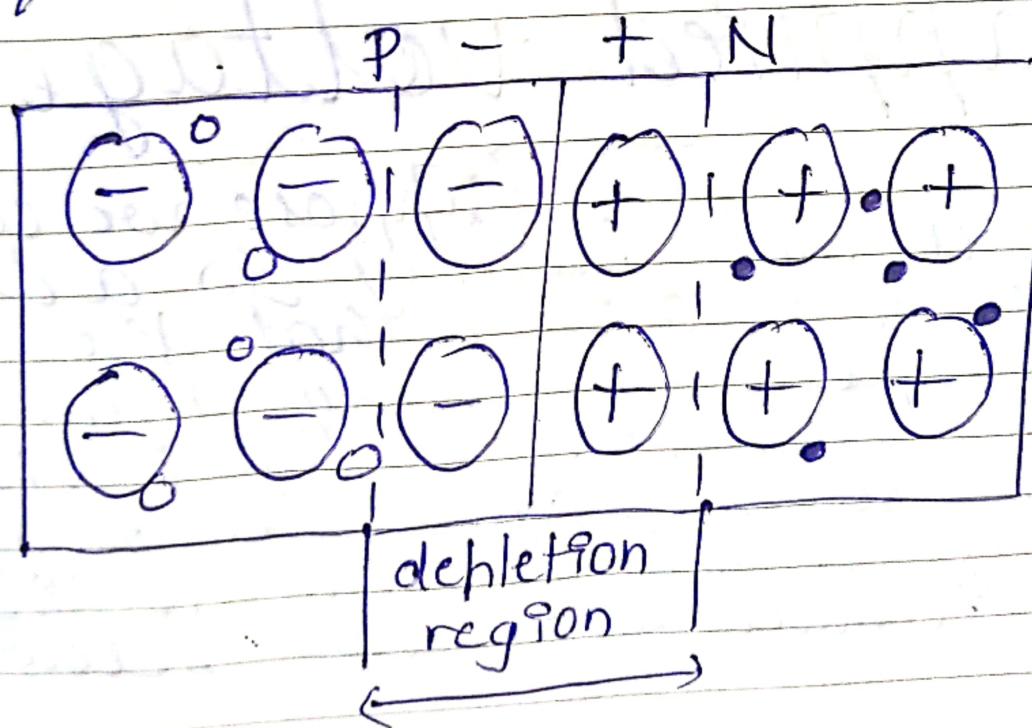

When you begin to think high idea emerges on its own.

12

SATURDAY • MARCH • 2016

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

The depletion region is also called the space charge region because it has immobile ions which are electrically charged, the depletion region works as a barrier and has a barrier potential of about $0.7V$ for silicon and about $0.3V$ for germanium diodes.

12

PN junction with applied voltage.

Suppose we connect an external battery to a diode in such a way that the positive battery terminal is connected to the P-side and anode and the negative battery terminal to the N-side or cathode as shown below then



Become a leader of that much potential that those who are walking ahead must also wait for your signal to act.


13

SUNDAY

APRIL 2016						
M	T	W	T	F	S	S
1	2	3				
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	

14

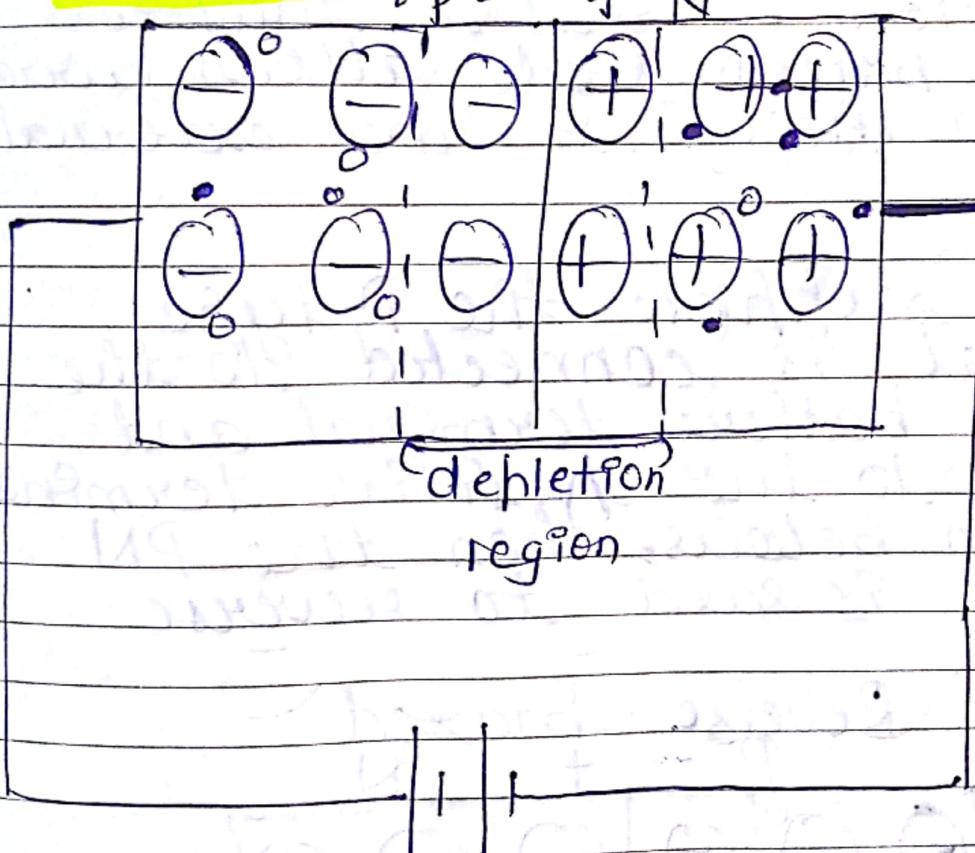The diode is said to be forward biased, in other words whenever the anode terminal is at a higher potential than the cathode the diode is forward biased.



With forward voltage barrier reduces and hence holes free electrons can cross



15



13-elect-I
16-elect-2

TUESDAY • MARCH • 2016

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

the junction) i.e. current flow can take place as the forward voltage is increased barrier decreases and when it exceeds the barrier potential the barrier is completely eliminated thus a forward biased diode allows current to flow through it and external circuit.


12

13

Suppose the P-type material is connected to the negative battery terminal and N-side to the positive terminal as shown below, then the PN junction is said to reverse biased.

Reverse biased

P - + N

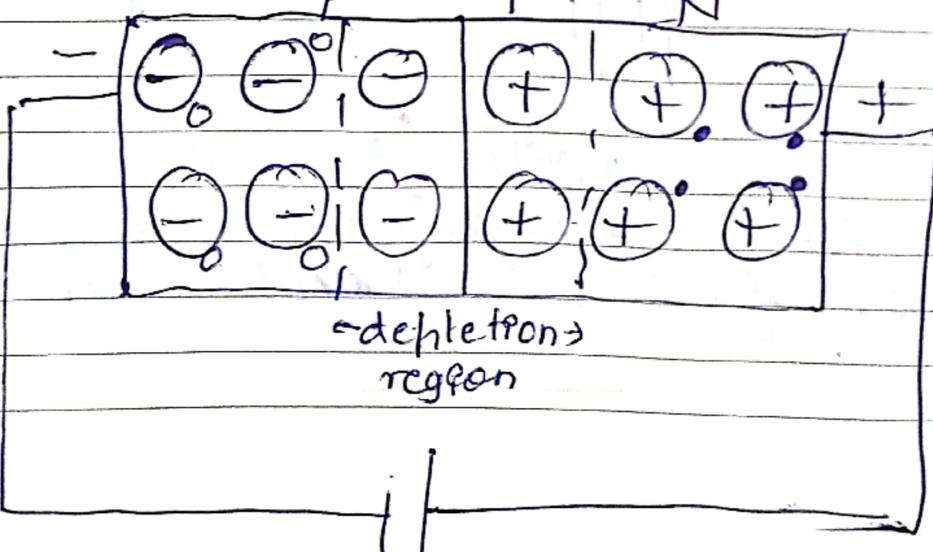

Get yourself loaded with bags of courage, hardwork and enthusiasm.

APRIL 2016						
M	T	W	T	F	S	S
1	2	3				
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	

WK 12 (076-290)

2016 • MARCH • WEDNESDAY

16

Whenever the P-side or the anode terminal of the diode is at a lower potential than N-side or cathode terminal then the diode is said to be reverse biased, here the reverse voltage simply increases the barrier and hence no current flows due to the majority charge carriers in both the regions, if reverse voltage is increased then there will still be no current through the diode. In other words a diode introduced in circuits allows current flow when it is forward biased and blocks the flow of current when it is reverse biased. A forward biased diode is said to be equivalent to a closed switch and reverse biased diode equivalent to an open switch.




Take dreams that you can turn into realities in future.

APRIL

MAY

17

THURSDAY • MARCH • 2016

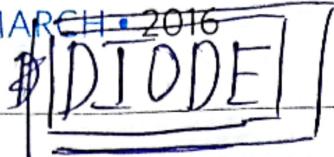

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

* A semiconductor device which has a single PN junction.

* It allows current when it is forward biased.

Absence of mobile carriers, holes and current carriers.

* Function:-


Forward biased

P type is connected to positive terminal and N type to negative terminal.

Reverse biased

P type is connected to negative terminal and N type to positive terminal.

Forward biased

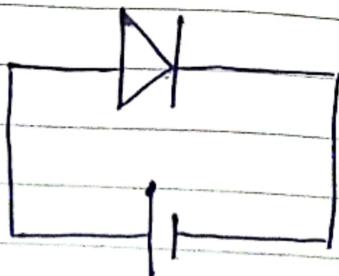


APRIL 2016
M T W T F S S
1 2 3
4 5 6 7 8 9 10
11 12 13 14 15 16 17
18 19 20 21 22 23 24
25 26 27 28 29 30

WK 12 (078-288)

2016 • MARCH • FRIDAY

18

Reverse biased

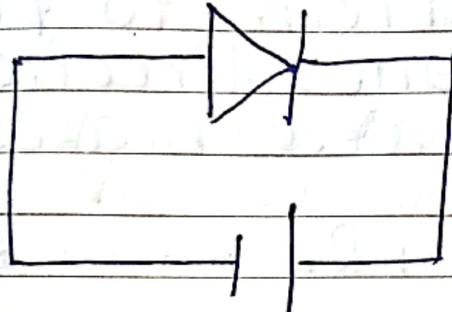

Explain diode: when it is just formed

when no external voltage is applied


Role played by depletion region

Behaviour of diode when voltage is applied to it.

Explanations should be with diagrams

Paper is easy

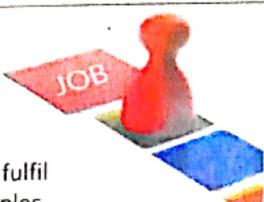If any part is not clear to you
I don't want anyone to fail
in this exam and score above
20.



A job is actually a program in which you have to fulfil their requirements based on your principles.

19

SATURDAY • MARCH • 2016

Important Property of a diode

8

- Diode allows current to flow through it in one direction when it is forward biased

10

$$\text{Series} \rightarrow R_s = R_1 + R_2 + R_3 + R_4 + \dots + R_n$$

11

$$\text{Parallel} \rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots + \frac{1}{R_n}$$

12

$$V = IR$$

2

$$H = I^2 RT$$

$$P = I^2 R$$

$$H = VIT$$

$$P = VI$$

3

$$H = \frac{V^2 T}{R}$$

$$P = \frac{V^2}{R}$$

20

SUNDAY

Try to get the full marks on the paper.
I-card is very-very important.



Remain consistent in your work success will follow.

APRIL 2016
M T W T F S S

1 2 3
4 5 6 7 8 9 10
11 12 13 14 15 16 17
18 19 20 21 22 23 24
25 26 27 28 29 30

21
~~21~~

Edward B. Surag

WK 13 (081-285)

2016 • MARCH • MONDAY

Paper II

21

Current flow through a reverse biased diode

When a diode is reverse biased no majority carriers can cross the junction since the barrier at the junction is increased due to reverse voltage, however minority carriers in the P and N regions can cross the junction and therefore a small current flows this current is small due to less no. of minority carriers the no. of minority carriers depends on temperature and not on voltage hence, increase in reverse voltage will not increase this reverse current.

V-I characteristics of a diode




22

TUESDAY • MARCH • 2016

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

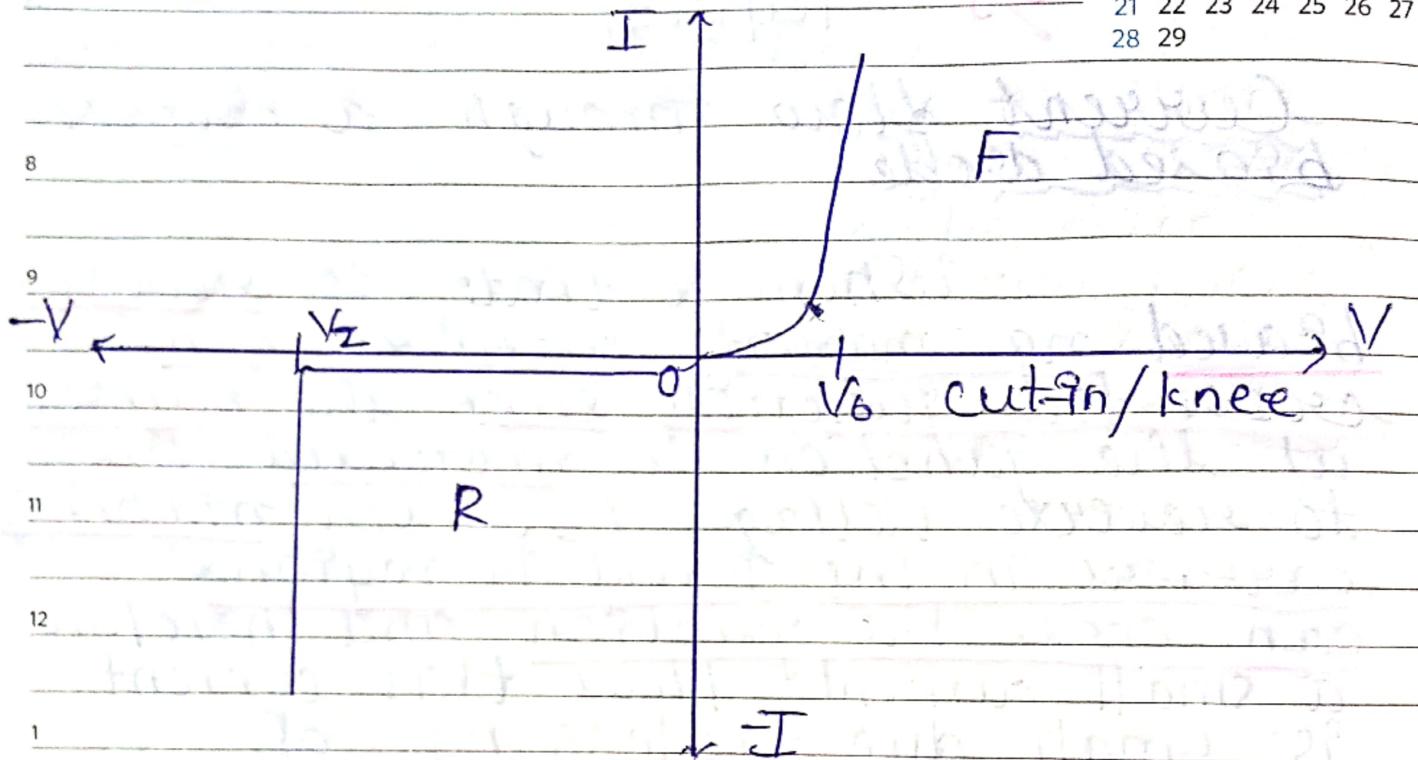

This is a graph between voltage applied across the diode terminals and the current that flows through it. This characteristic tells us how much current flows for a particular value of diode voltage.

① FORWARD CHARACTERISTICS

This is the characteristic which is obtained when the



Work within your potential, if more increase your potential not your work.

APRIL 2016
M T W T F S S
1 2 3
4 5 6 7 8 9 10
11 12 13 14 15 16 17
18 19 20 21 22 23 24
25 26 27 28 29 30


23 MARCH

WK 13 (083-283)

2016 • MARCH • WEDNESDAY

23

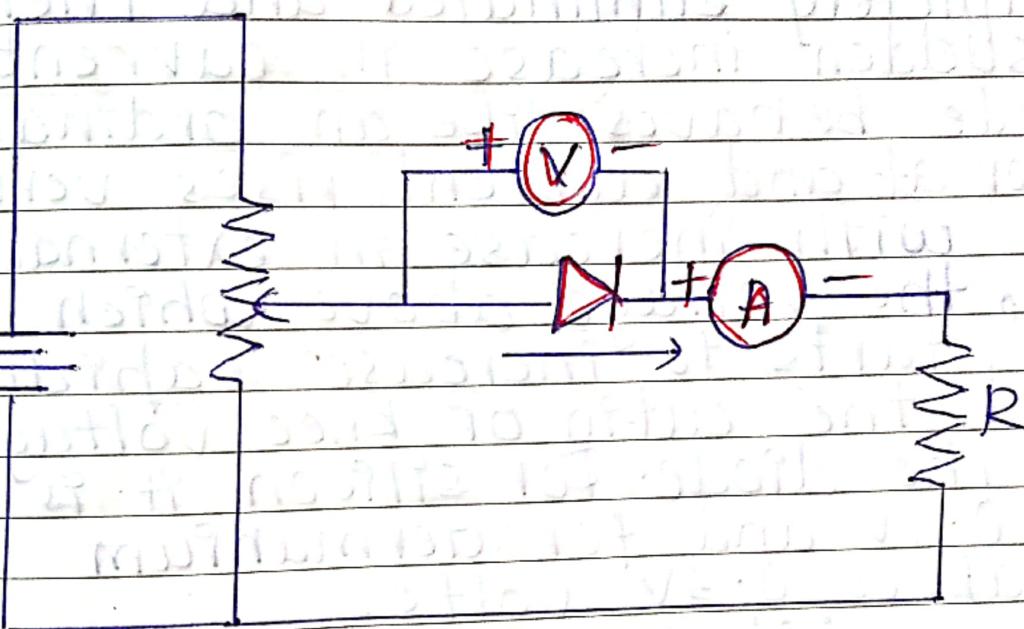applied voltage forward biases the diode, to obtain this we make use of the foll. circuit.



Each value of diode voltage produces a particular current initially when the applied voltage takes value of 0.1V or 0.2V the diode current is very small the diode does not conduct well until the external voltage overcomes the barrier potential therefore in the case of silicon



Keep your focus positive on family and career as well coz both has to move till end with.

THURSDAY • MARCH • 2016

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

24

- as we approach $0.7V$
 a no. of holes and free e^- start
 crossing the junction as the barrier
 is reduced, above $0.7V$ the barrier
 is completely eliminated and there
 is a sudden increase in current.
 The diode behaves like an ordinary
 conductor at and current rises very
 sharply with increase in external
 voltage, the voltage above which the
 current starts to increase rapidly
 is called the cut-in or knee voltage
 (V_0) of the diode. For silicon it is
 above $0.7V$ and for Germanium
 it is above $0.3V$ volts.

when

Reverse Characteristic


When a diode is reverse biased the relation betn
 reverse voltage and resulting
 current is shown by the reverse
 characteristic, the foll circuit is
 used to plot the reverse characteris-
 tic.



Your level of thinking increases with growing experience not with growing age.

APRIL 2016						
M	T	W	T	F	S	S
1	2	3				
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	

25

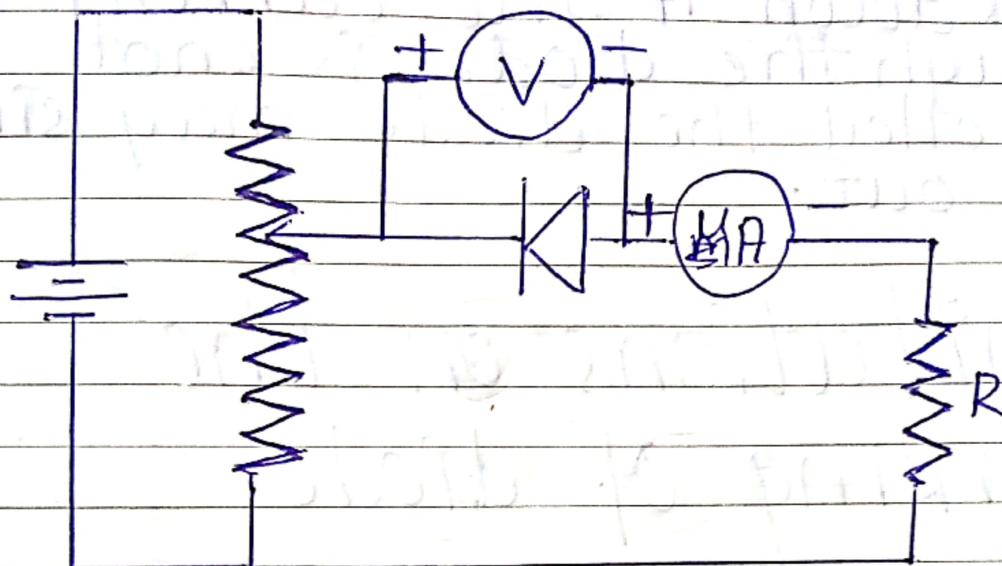

In the reverse biased condition as you increase the applied voltage the current remains small and constant for all voltages upto a certain limit because this current is due to the minority carriers which are thermally generated, when the voltage is made too high the current through the diode increases rapidly this voltage at which this phenomenon occurs is called the breakdown voltage



26

SATURDAY • MARCH • 2016

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

(V_z) of the diode at breakdown if the current through the diode is not controlled the diode may simply burn out.

Limitations on the working of diode.


(i) Max. forward current (I_{Fmax})

If the current through a diode is very large excessive heat generated will destroy the diode hence the manufacturer of the diode specifies

27

SUNDAY

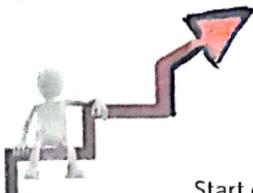the max. current a diode can safely handle without any damage to it, when forward biased.



Start designing your goal with a focussed vision.

APRIL 2016
M T W T F S S
1 2 3
4 5 6 7 8 9 10
11 12 13 14 15 16 17
18 19 20 21 22 23 24
25 26 27 28 29 30

WK 14 (088-278)

2016 • MARCH • MONDAY

28

Peak Inverse Voltage (PIV rating)

It is defined as the max voltage that a diode can withstand when reverse biased before breakdown occurs.

Max. Power Rating

It is the max power that a PN junction can withstand without causing damage to it.

Application of diode

rectifier



The signal to go must comes from your mind
nobody else will turn the light green.

APRIL

MAY

29

TUESDAY • MARCH • 2016

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

Rectifiers are circuits which convert AC to DC due to the property of allowing current flow in only one direction. It is possible to use a diode for converting AC to DC. There are 3 types of Rectifiers half wave, full wave and bridge rectifier. The circuit diagram of a half wave rectifier is shown below, it uses step-down transformer for converting the high AC mains voltage to a lower one. Diode is used as a the rectifier and the output is delivered to a load resistor R_L .

Half wave rectifier




Make a rigid plan for your success,
enormous flexibility sometimes makes you face failure.

APRIL 2016						
M	T	W	T	F	S	S
1	2	3				
4	5	6	7	8	9	10
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	

WK 14 (090-276)

2016 • MARCH • WEDNESDAY

30

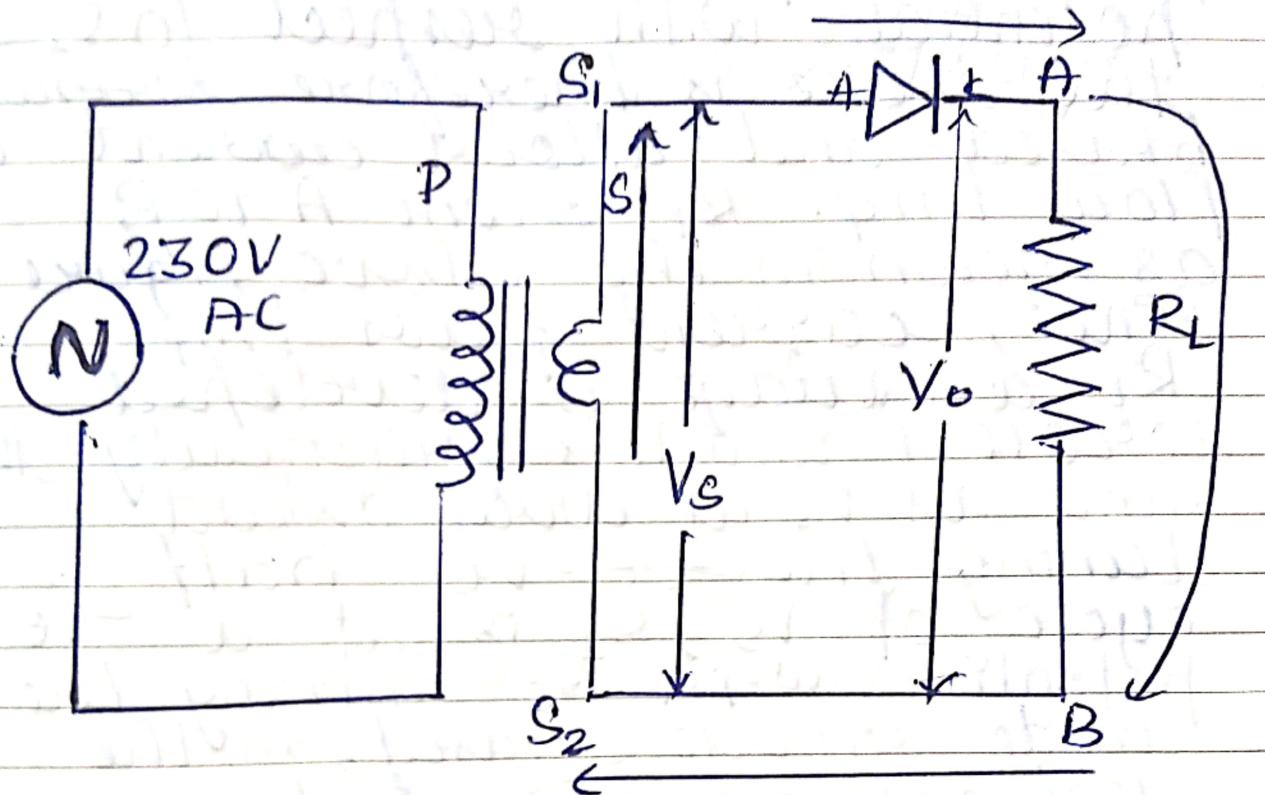

230V AC is applied to the primary terminals of the transformer, the secondary terminals S₁ and S₂ are connected in series with the diode and the load R_L. The transformer secondary provides a voltage V_S to the rectifier. During the pos. half cycle of the secondary voltage V_S

ADWAIT S. PURAO



31

THURSDAY • MARCH • 2016

FEBRUARY 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29					

S₁ is at a positive potential with respect to S₂.
 the diode is therefore forward biased and allows current to flow thro. R_L from A to B as shown in the above figure.
 Since, current flows thro. R_L a voltage is developed across it which is practically the same as V_s at every instant during the +ve half cycle of V_s, S₁ is at a -ve potential w.r.t S₂ making the diode reverse biased, in the ideal case no current flows through the reverse biased diode and hence no current through R_L with output voltage equal to zero we can conclude that when V_s is going thro. its +ve half output V_o is also going through its positive half cycles but when V_s is in its negative half V_o remains constant at 0.




Discuss to generate ideas not to win arguments.

1

FRIDAY • APRIL • 2016

MARCH 2016						
S	M	T	W	T	F	S
				1	2	3
				4	5	6
				7	8	9
				10	11	12
				13	14	15
				16	17	18
				19	20	21
				22	23	24
				25	26	27
				28	29	30
				31		

this is shown on the wave forms below:

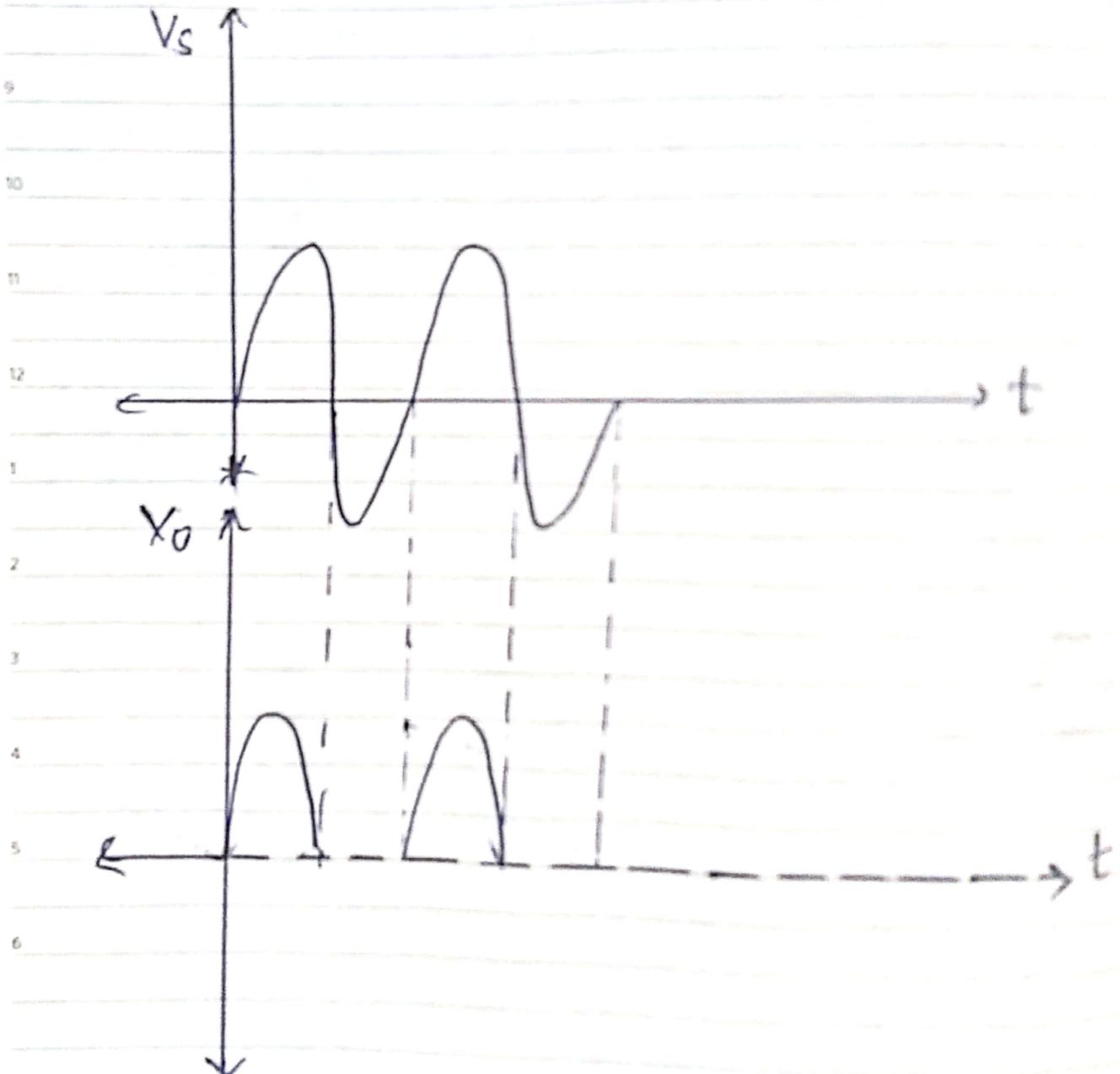

Opportunities falls in your hand use it and then the other one will fall

MAY 2016

M	T	W	T	F	S	S
30	31			1		
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29


WK 14 (093-273)

2016 • APRIL • SATURDAY

2

Output V_o changes in magnitude but is unidirectional hence we say that the output of the a rectifier is not a perfect DC.

Centre tapped full wave

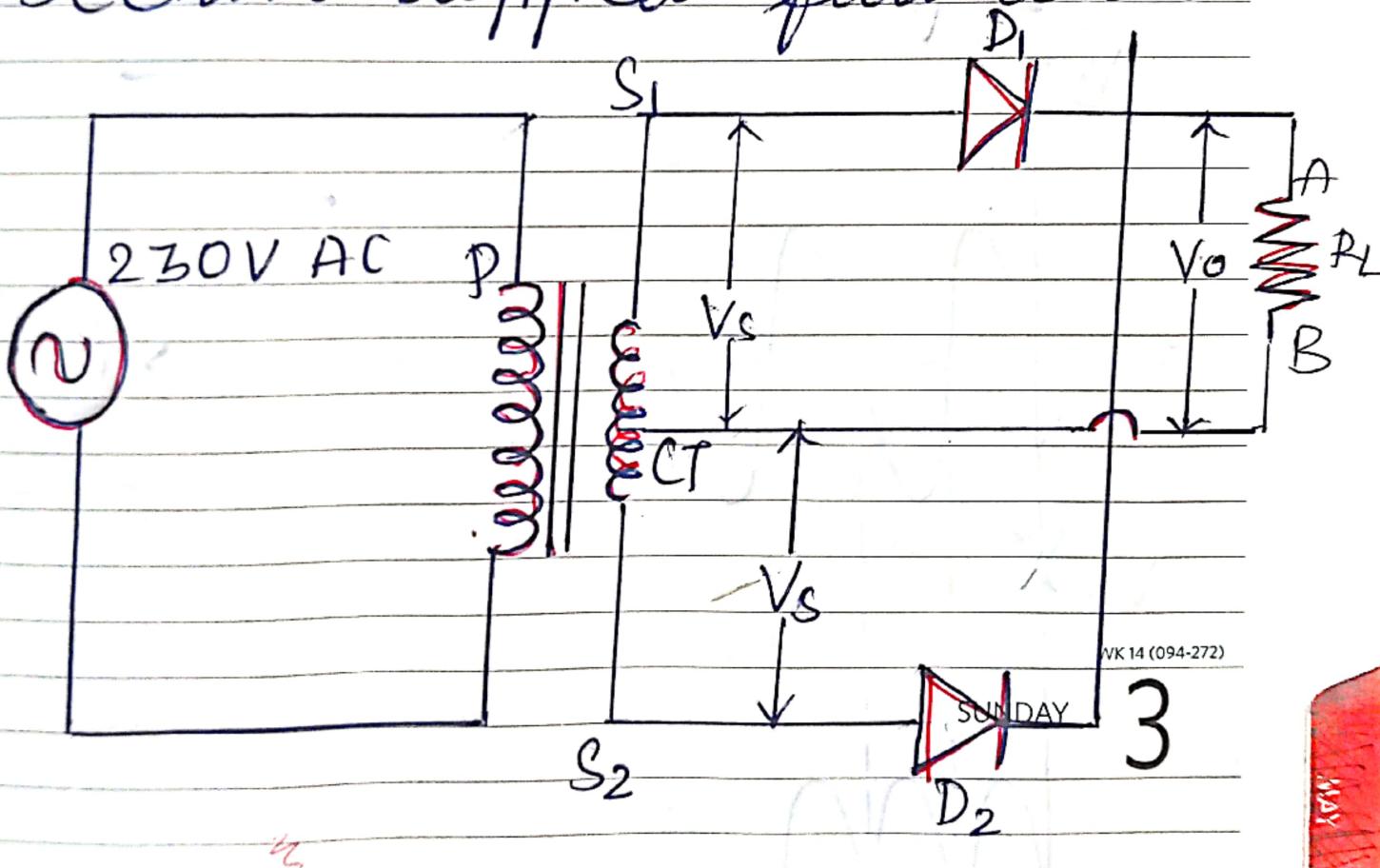

WK 14 (094-272)

3





4

MONDAY • APRIL • 2016

MARCH 2016

S	M	T	W	T	F	S
	1	2	3	4	5	
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

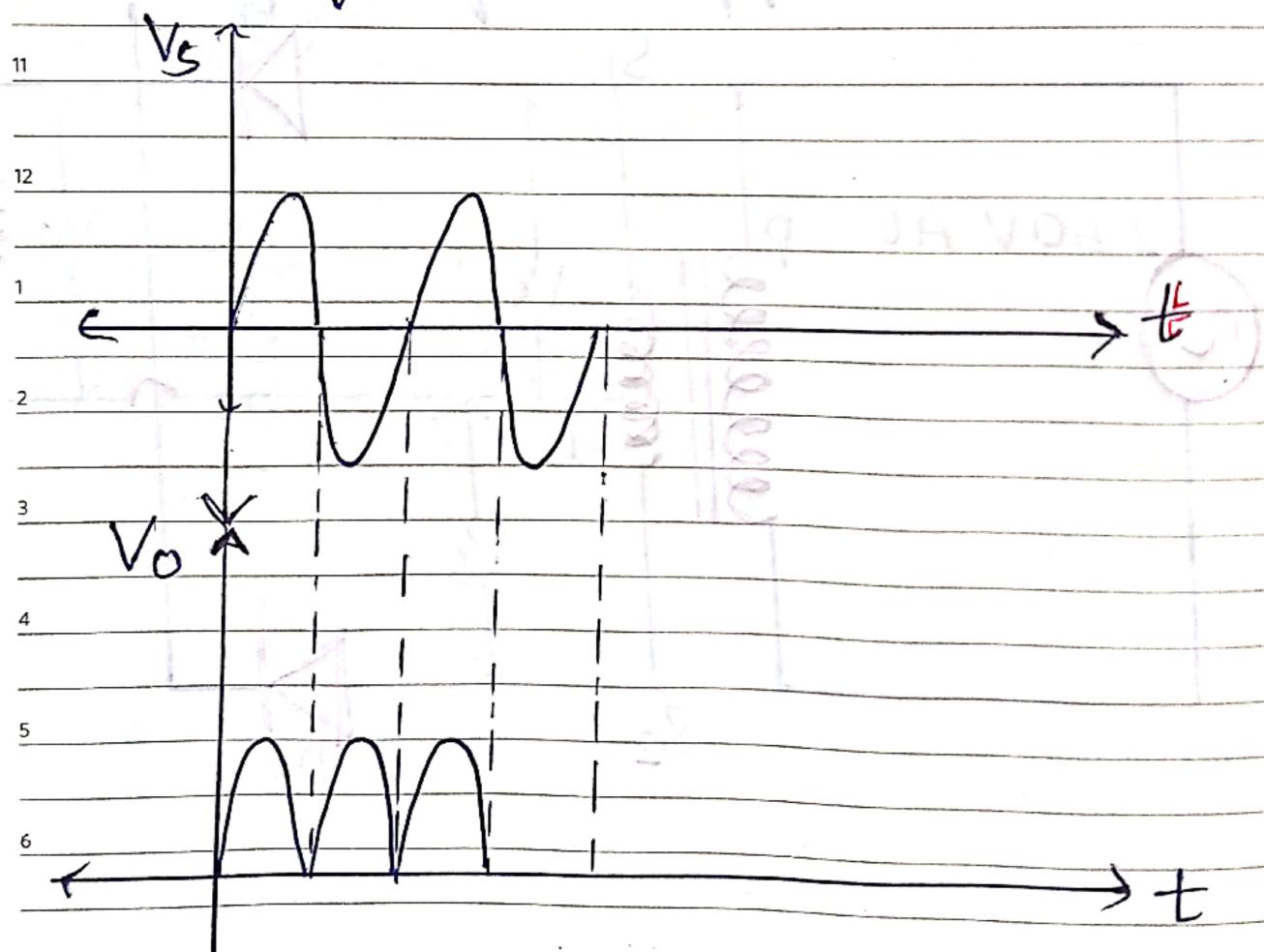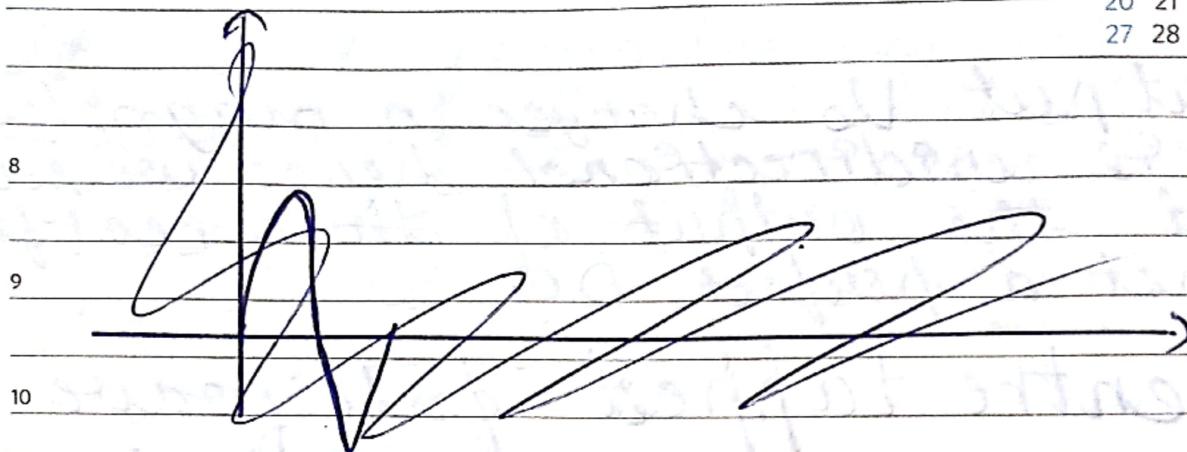

Achievement is not reaching from one point to other
but overcoming all the obstacles coming in the way.

M	T	W	T	F	S	S
30	31				1	
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

2016 • APRIL • TUESDAY

5

This circuit makes use of a ~~center-tapped transformer~~ and two diodes D_1 and D_2 due to the ~~center-tap~~ (CT) when S_1 terminal becomes positive w.r.t CT the other terminal S_2 becomes as much negative w.r.t CT after half a cycle the position is reversed V_S is the secondary voltage of the transformer between terminals S_1 and CT and S_2 and CT during the +ve half cycle of V_S , S_1 is at a +ve potential w.r.t CT and S_2 is at a -ve potential w.r.t CT, \therefore diode D_1 is forward biased and diode D_2 is reverse biased, current flows thro. D_1 , load R_L from A to B and the upper half of the secondary winding, since current flows thro. R_L a voltage is developed across it which is practically the same V_S at every instant. During the



6

WEDNESDAY • APRIL • 2016

MARCH 2016						
S	M	T	W	T	F	S
			1	2	3	4
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

negative half cycle of V_s
 S₁ is at a negative potential and S₂
 is at a positive potential w.r.t CT
 hence D₁ is reverse biased and
 D₂ forward biased, current flows
 thro' D₂ load R_L from A to B and
 the lower half of the secondary
 winding, current flowing thro'.
 R_L develops a voltage across it,
 which is almost the same as
 V_s at every instant, from the
 input output wave forms we
 observe that output changes
 in magnitude but is unidirectional,
 hence output of this rectifier
 is also not a perfect DC.

Bridge Rectifier



A true friend is one who unlocks your best qualities
 from which you are still unaware.

MAY 2016


M	T	W	T	F	S	S
30	31				1	
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

WK 15 (098-268)

2016 • APRIL • THURSDAY

7

Diagram

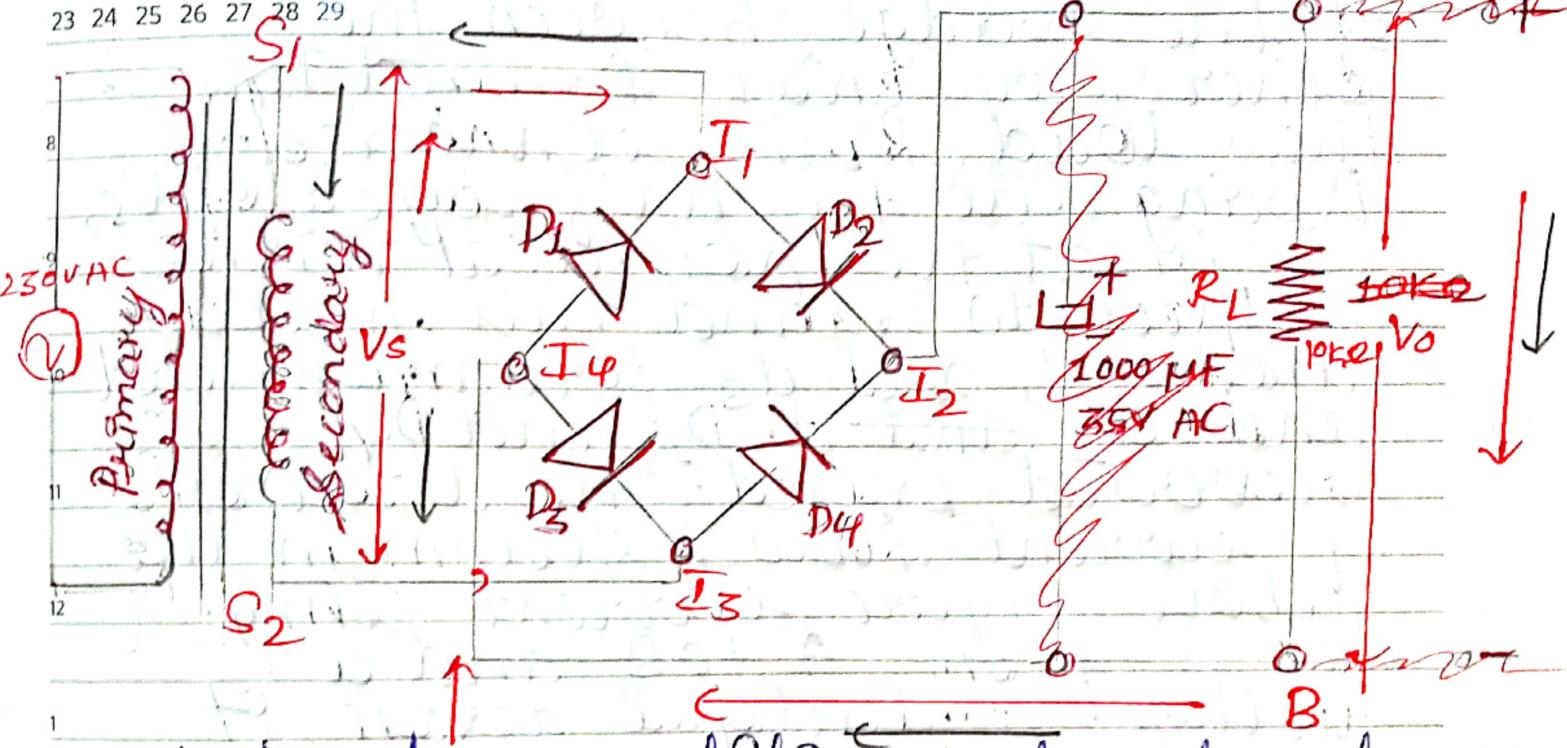

A bridge rectifier also produces full wave rectification It differs from a centre tap full wave rectifier in the respects:

- 1) It uses four diodes and secondly it does not need centre tap transformer, 230 V AC is applied to the primary terminals of the step down transformer.
- 2) The secondary voltage V_s is applied to the diagonally opposite ends T_1 and T_3 of



8

FRIDAY • APRIL • 2016

and

of the bridge between the other two ends T_2 and T_4 , the load R_L is connected.

During the first half cycle of V_S , T_1 is at +ve potential with respect to T_3 and this makes diodes d_1 and d_3 forward biased and d_2 and d_4 , D_2 and D_4 reversed biased. The direction of current flow is shown in the above figure, current thru.

R_L is from A to B and a voltage is developed across it which is almost the same as V_S at every instant. During the half cycle of V_S , T_1 is made -ve with respect to T_3 . \therefore diodes D_1 , D_3 are reversed biased while diodes D_2 and D_4 are forward biased, current flows along the path shown by a pencil (\rightarrow)

Current thru. R_L is



One who saves in the present, enjoys the future.


MAY 2016						
M	T	W	T	F	S	S
30	31			1		
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

WK 15 (100-266)

2016 • APRIL • SATURDAY

9

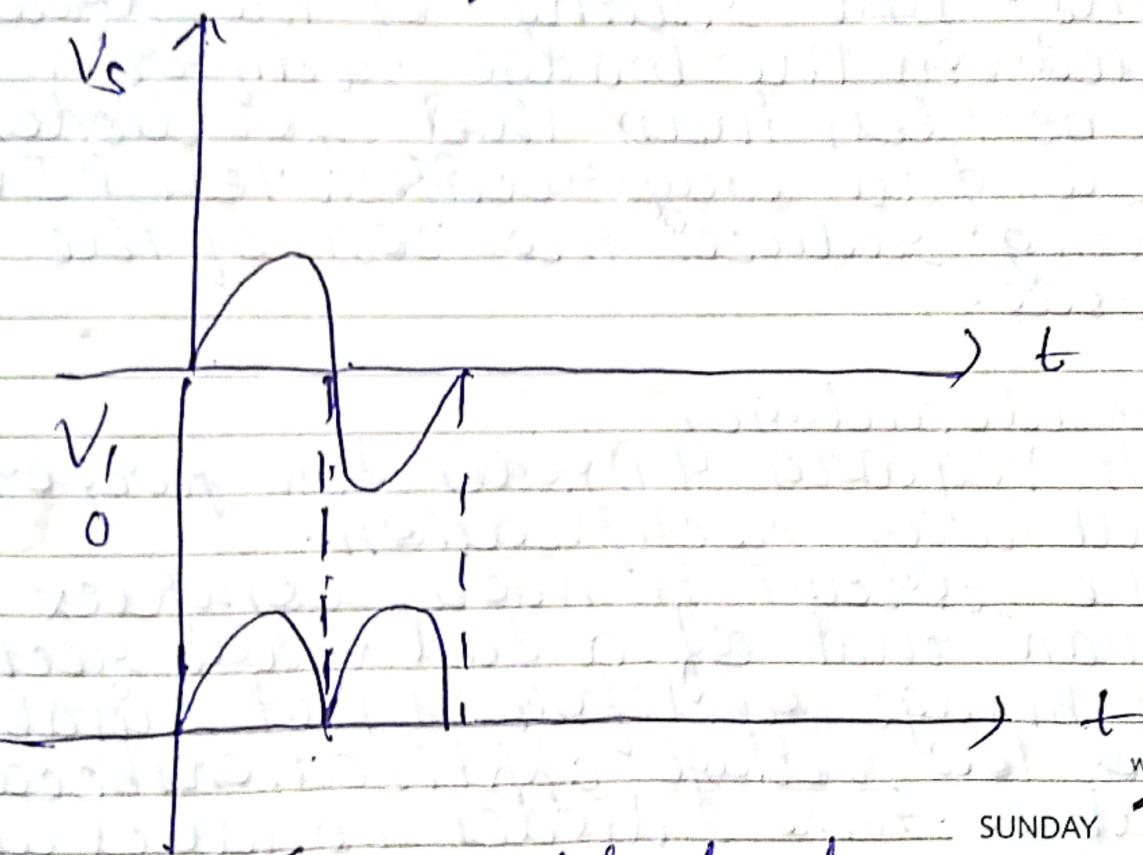again in the same direction A to B and a voltage V_o is developed across R_L which is practically the same as V_s at every instant. The input and output wave forms are shown below.



WK 15 (101-265)

SUNDAY

10

The output of a bridge rectifier is also not a perfect DC becoz because even though it is unidirectional it still changes in magnitude.



11

MONDAY • APRIL • 2016

MARCH 2016

S	M	T	W	T	F	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

Advantages

- 1) It does not require centre tapped secondary winding for the transformer which is more costly.
- 2) The PIV rating of the diodes used in the bridge rectifier is to be less than that for diodes in a full wave rectifier; less PIV rating reduces the cost of the diode.

Disadvantages

- 1) It requires 4 diodes for performing full wave rectification.
- 2) The circuit is more complex than that of a full wave rectifier.
- 3) A bridge rectifier is not suitable for low voltage applications because at a time, 2 diodes conduct and the voltage across them becomes significant.



MAY 2016

M	T	W	T	F	S	S
30	31				1	
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

WK 16 (103-263)

2016 • APRIL • TUESDAY

12

