

1

MONDAY • AUGUST • 2016

## Part -II


S	M	T	W	T	F	S
31					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

UJT (Unijunction Transistor)

8

Unlike a BJT a UJT has a single PN junction. It is a semiconducting device which shows a negative resistance effect and hence it can be used to generate a sawtooth waveform.


12

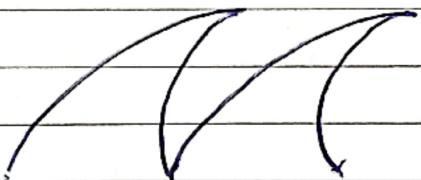

1
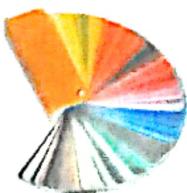
## 2 Construction:

It basically consists of a N-type silicon region with a P-type region diffused into it creating a single PN junction. The P region is a heavily doped region compared to the N regions, two terminals base-2 ( $B_2$ ) and base-1 ( $B_1$ ) are connected to the N region while the third terminal



Its upto you what colours you will fill in the blank sheet of your life.

SEPTEMBER 2016

M	T	W	T	F	S	S
1	2	3	4			
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

WK 32 (215-151)


2016 • AUGUST • TUESDAY

2

emitter is taken out from the P-region.

Base-2


$B_2$

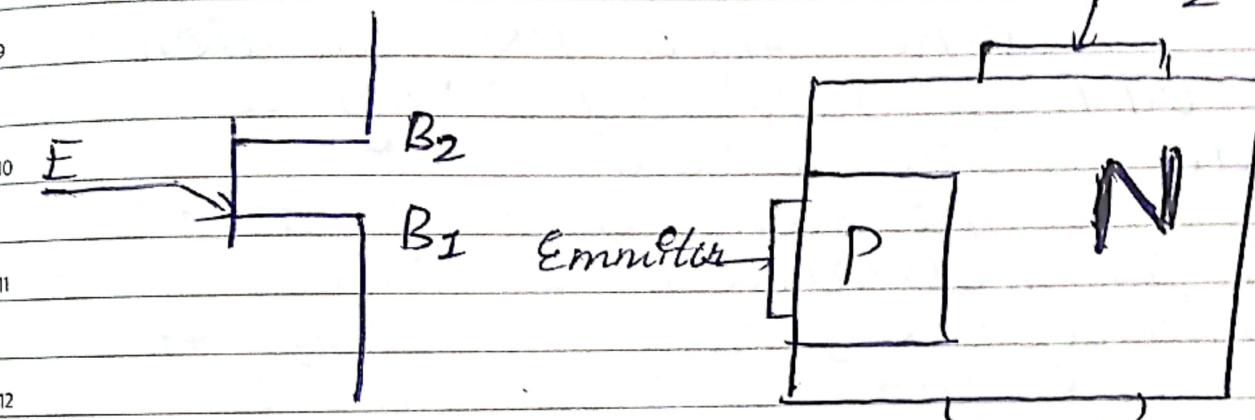

Symbol

Base-1  
 $B_1$

Equivalent circuit

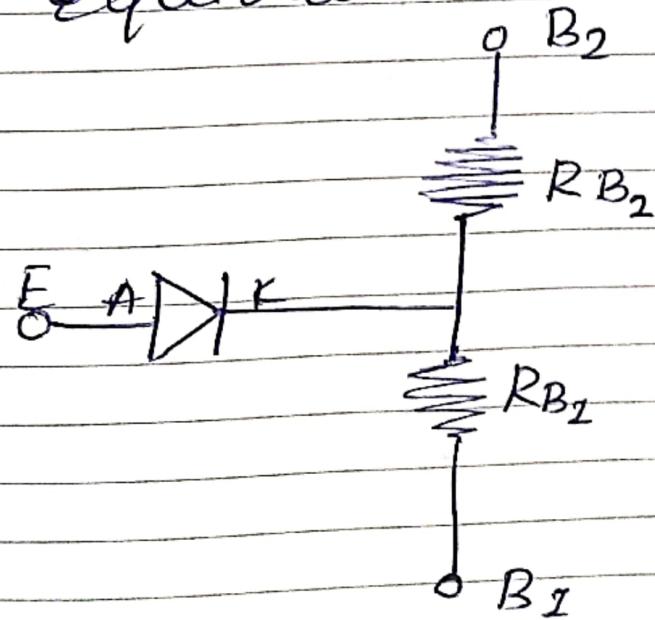

Nobody can answer success, it is just a matter of question.

3

WEDNESDAY • AUGUST • 2016

JULY 2016


S	M	T	W	T	F	S
31					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

In order to understand the working of a UJT we study its equivalent circuit which is shown above.

The single PN junction in a UJT is represented by a diode in the circuit.

The resistance of the UJT is indicated by 2 series resistances  $R_{B_2}$  and  $R_{B_1} + R_{B_2}$ .  
 12 the resistance of the base-2 portion of Emitter to base to resistance  $R_{B_1}$  indicates emitter to  $B_1$  resistance or resistance of base-1 portion, with no voltage applied to the UJT the inter-base resistance  $R_{BB} = R_{B_1} + R_{B_2}$ .

#### Working

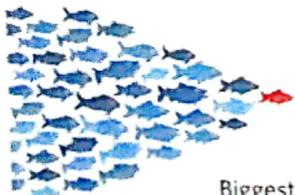

Bigest responsibility of leader is to guide the followers to the right destination.

SEPTEMBER 2016


M	T	W	T	F	S	S
			1	2	3	4
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

WK 32 (217-149)

2016 • AUGUST • THURSDAY

*August 28 ~*

4

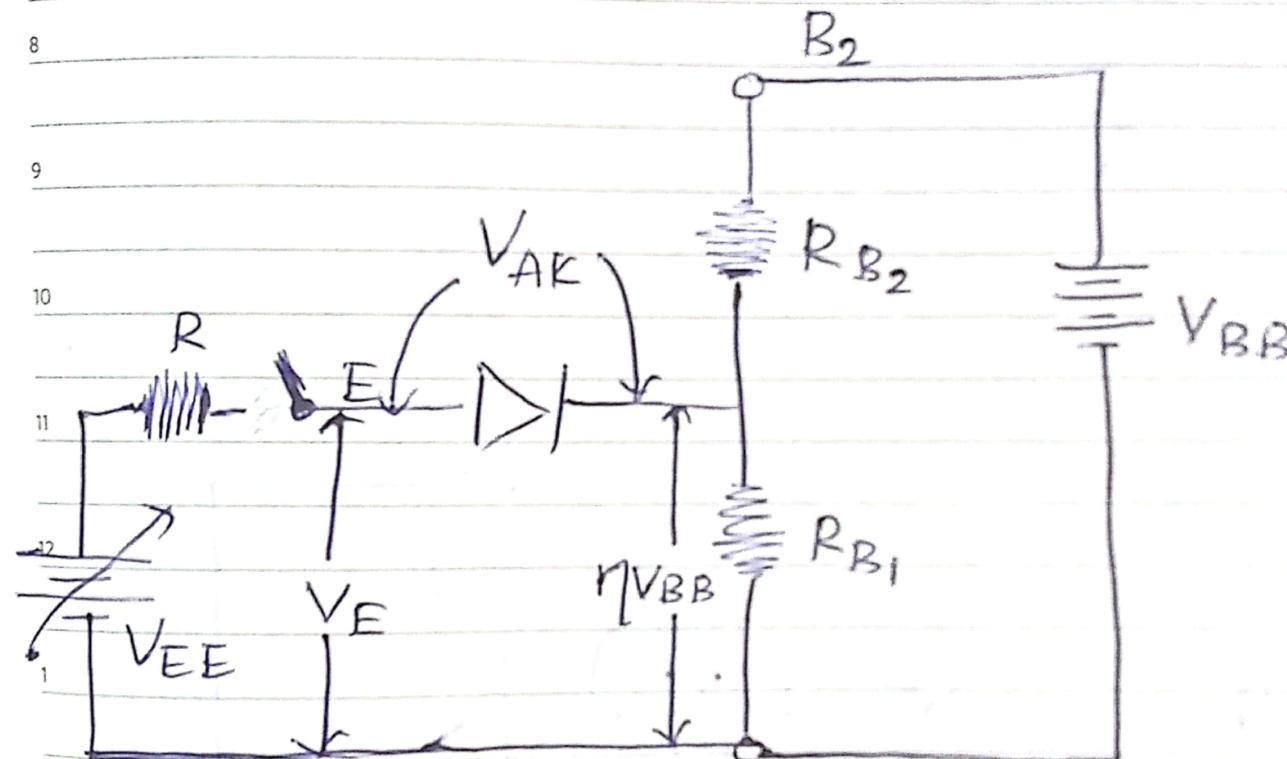

Scanned with OKEN Scanner


5

FRIDAY • AUGUST • 2016

B η

S	M	T	W	T	F	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

8

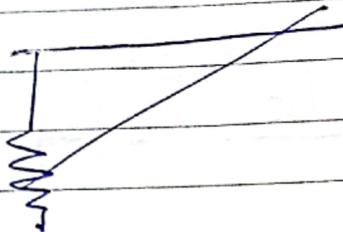

9

10

11


12

1

2

3

4

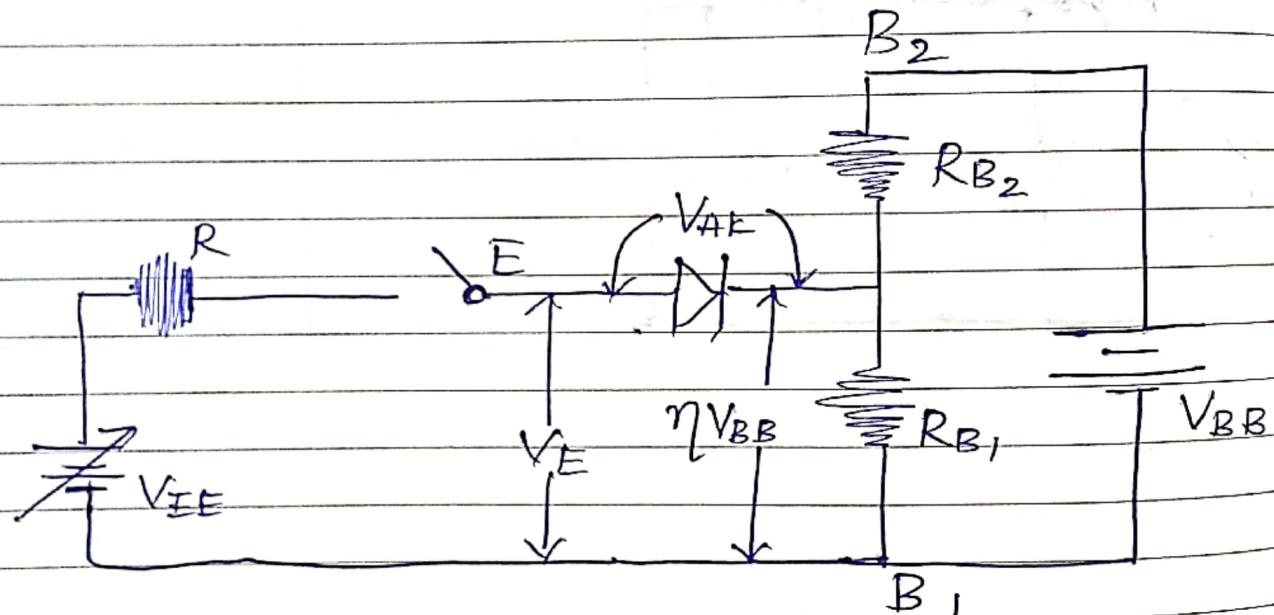

Suppose a voltage

$V_{BB}$  is applied between the two bases with no voltage given to the emitter i.e. the switch is open, in this case the voltage  $V_{BB}$  divides up across  $R_{B1}$  and  $R_{B2}$  so that the voltage



SEPTEMBER 2016

M	T	W	T	F	S	S
1	2	3	4			
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

WK 32 (219-147)

2016 • AUGUST • SATURDAY

6

across  $R_B$ ,  $R_E$   $\frac{R_B}{R_B + R_{B_2}} \times V_{BB}$

$= \frac{R_B}{R_{BB}} \times V_{BB}$

$P_{o-d} \eta V_{BB} \quad \therefore \eta = \frac{R_B}{R_B + R_{B_2}}$

(It is the

entrance stand off  
ratio & its value  
lies between 0.51 and  
0.92)

The voltage  $\eta V_{BB}$  across  $R_B$ , reverse biases the diode since cathode potential equal to  $\eta V_{BB}$  is greater than anode potential. As a result negligible current flows through the diode and hence through the VJT. If now a progressive voltage is applied to the emitter (switch closed) the diode will become forward biased when the emitter



Move forward with certainty, give up all your doubts.

WEEK 32

SEPTEMBER

DECEMBER



Scanned with OKEN Scanner

8

MONDAY • AUGUST • 2016

JULY 2016

S	M	T	W	T	F	S
31				1	2	
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

or anode voltage exceeds  $\eta_{V_{BB}}$   
 for a voltage  $\eta_{V_{BB}} + 0.1$  the  
 diode is forward biased  
 with a voltage of  $0.1\text{ V}$  across  
 its terminals, hence a small  
 forward current flows, this  
 increases as the supply  $V_E$  is  
 increased but when the  
 emitter voltage reaches the  
 value  $\eta_{V_{BB}} + 0.7$  the diode becomes  
 properly forward biased with  
 $0.7\text{ volts}$  across it, for this  
 condition a large current flows  
 P-holes are injected from P-type  
 to N-type region, these holes  
 move towards the B<sub>1</sub> terminal &  
 flooding of the lower portion of  
 the N-region with holes indicated  
 $R_{B_1}$  decrease by a large range.  
 For such a large drop in  $R_{B_1}$ ,  $V_E$   
 decreases, this is the negative  
 resistance effect where an attempt  
 to increase  $I_E$  decreases  $V_E$ .


SEPTEMBER 2016

M	T	W	T	F	S	S
1	2	3	4			
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

WK 33 (222-144)

2016 • AUGUST • TUESDAY

9

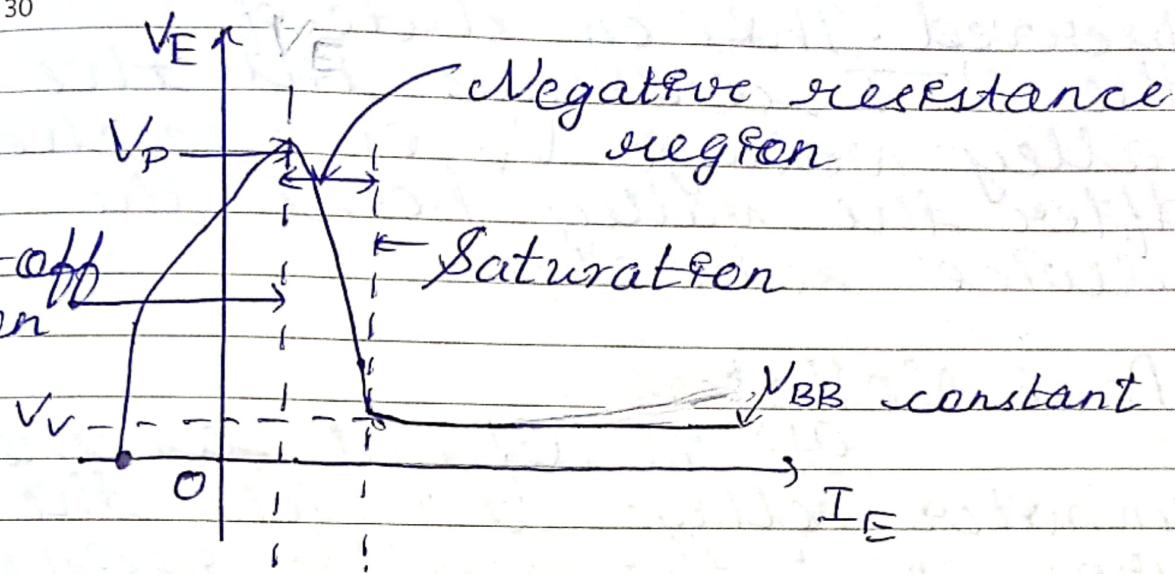

The above curve shows the relation between emitter voltage  $V_E$  and emitter current  $I_E$  when a constant voltage  $V_{BB}$  is applied between the bases. When  $V_E$  equals zero the diode is reverse biased & a small reverse current flows which is shown in the characteristic. As long as  $V_E < \eta V_{BB}$ , diode is reverse biased and the reverse current flows. However when  $V_E$  reaches the peak voltage

$V_P = \eta V_{BB} + 0.7$ , the diode becomes properly forward biased & negative resistance effect is

10

WEDNESDAY • AUGUST • 2016

S	M	T	W	T	F	S
31					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

observed. This on state of the UJT continues till the valley voltage  $V_v$  is reached. After the valley point the device saturates.

## 10 Peak Voltage


It is defined as the emitter voltage at which the UJT turns on & the negative resistance effect is observed.

It is given by the expression

$$V_p = \eta V_{BB} + 0.7$$

where  $\eta V_{BB}$  is called the stand off voltage.

## 4 sawtooth generator

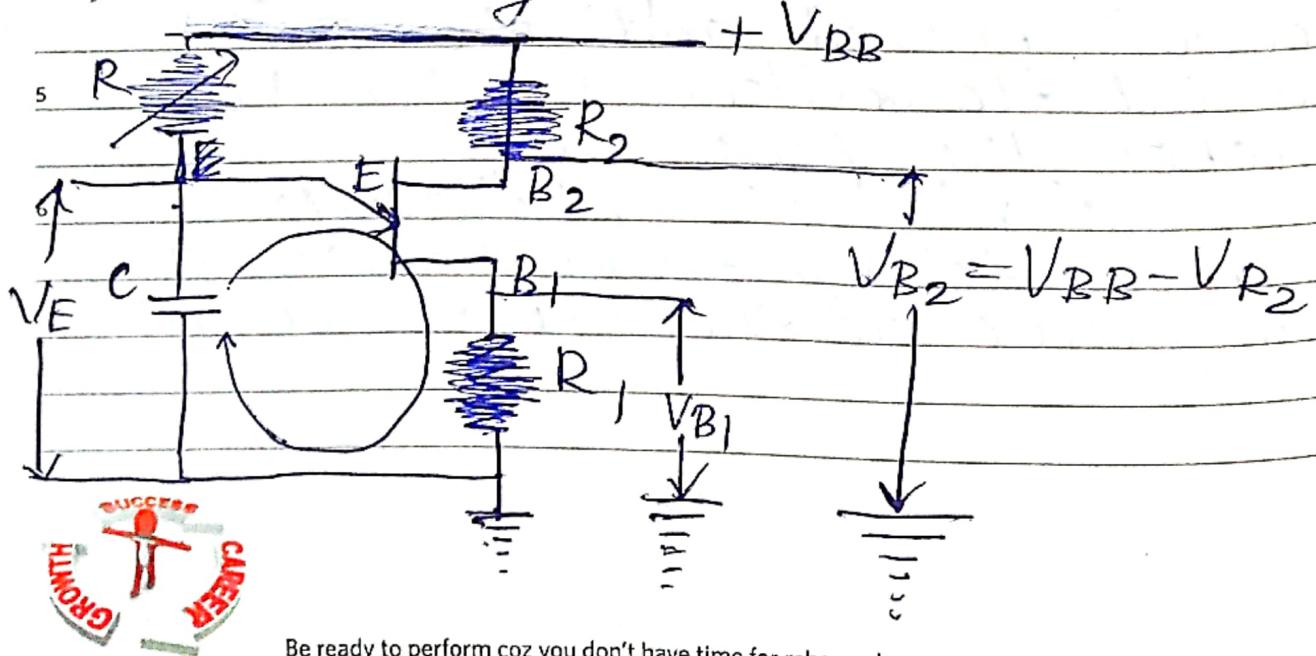

Be ready to perform coz you don't have time for rehearsals.



SEPTEMBER 2016

M	T	W	T	F	S	S
1	2	3	4			
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		


WK 33 (224-142)

2016 • AUGUST • THURSDAY

11

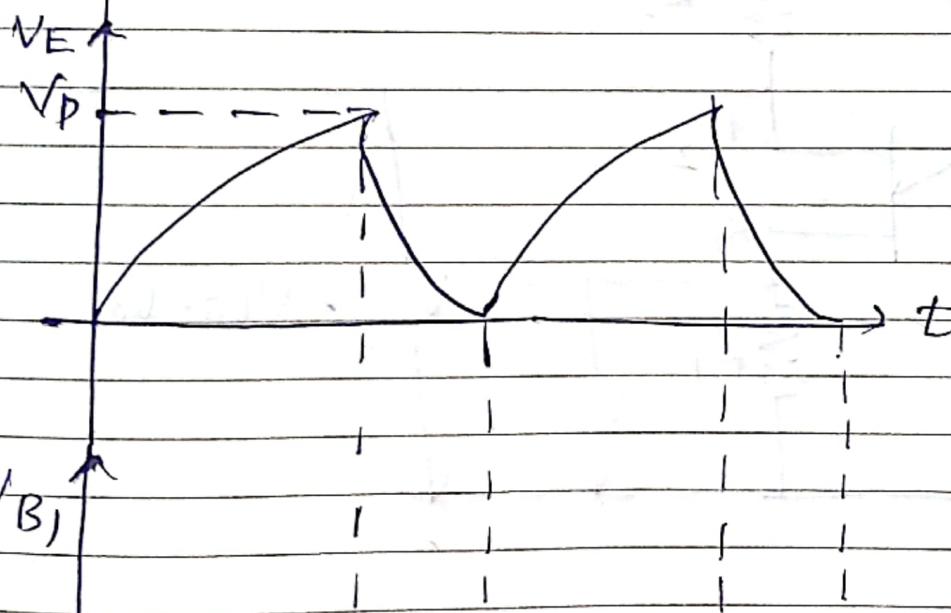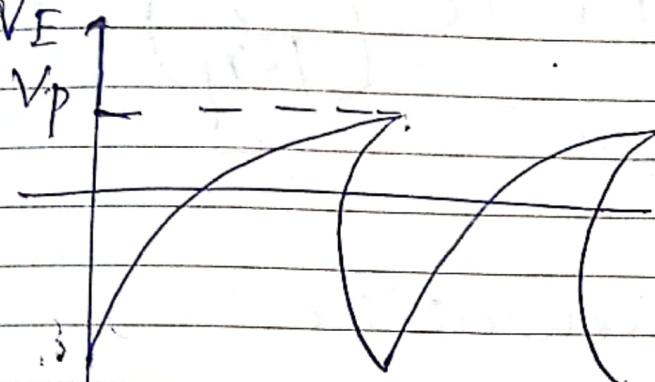

Positive  
spike

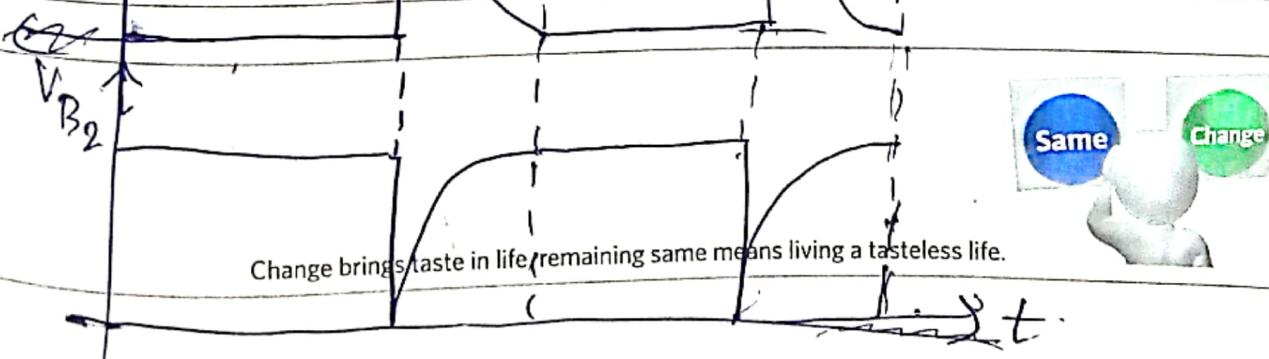

Scanned with OKEN Scanner

SEPTEMBER

OCTOBER

DECEMBER

12

FRIDAY • AUGUST • 2016

$$T = 2.303 RC \log \left( \frac{1}{1-\eta} \right)$$


8

$$f = \frac{1}{T}$$

9

## Sawtooth generator

10

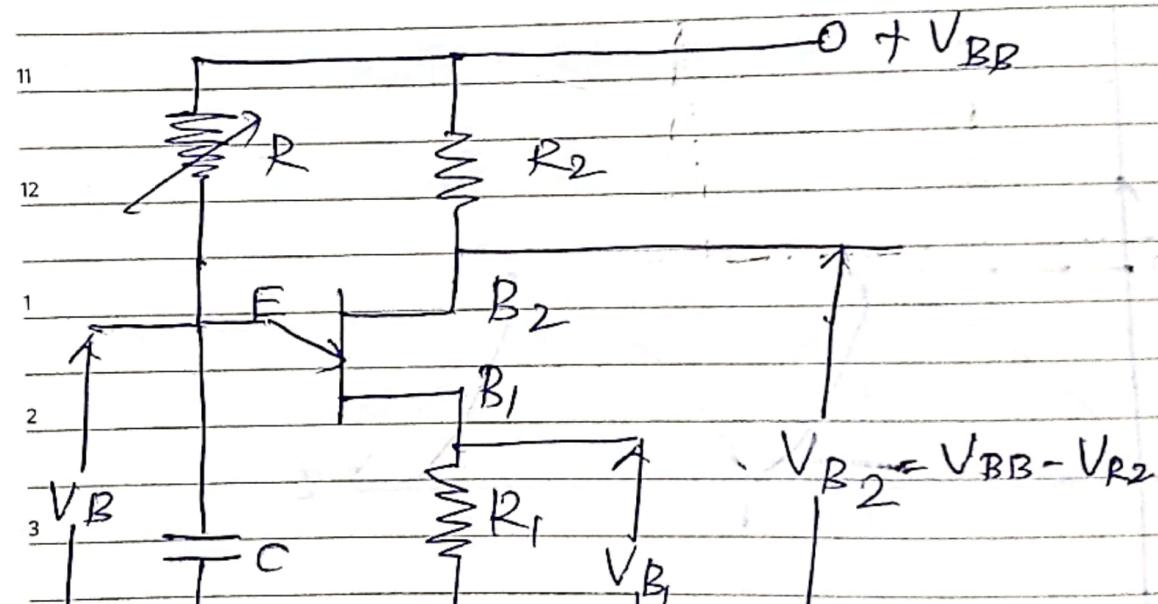

Build your confidence, give up your fear of being wrong.

S	M	T	W	T	F	S
31						1 2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

SEPTEMBER 2016

M	T	W	T	F	S	S
1	2	3	4			
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

WK 33 (226-140)

2016 • AUGUST • SATURDAY

13

V<sub>E1</sub>V<sub>P</sub>V<sub>B1</sub>V<sub>B2</sub>

t

t

→

WK 33 (227-139)

SUNDAY

14

A VJT sawtooth generator or oscillator circuit is a circuit that generates an



Think positive sometimes it makes impossible into possible.



Scanned with OKEN Scanner

 NOVEMBER  
 DECEMBER

15

MONDAY • AUGUST • 2016

S	M	T	W	T	F	S
31				1	2	
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

AC output (sawtooth without the help of an input AC signal) and working with only a DC power supply

## Working

When the supply  $V_{RB}$  is turned on the UJT is in the off state & the capacitor begins to charge through the series resistance  $R$  during the charging period. The voltage across the capacitor rises in an exponential manner until it reaches the peak voltage of the UJT. This capacitor voltage is emitter voltage of for UJT. Hence when the peak value is reached the UJT turns on and provides a path for the capacitor to discharge. The capacitor discharges through the UJT &  $R$ , when it discharges its voltage  $V_{CE}$  decreases & when it



Success comes to those who goes out and works for it.

M	T	W	T	F	S	S
1	2	3	4			
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

2016 • AUGUST • TUESDAY

16

reaches a certain low value the  
 1 vato UJT turns on again & the  
 2 capacitor begins to charge, this  
 3 process continues over & over  
 4 again & a sawtooth wave is  
 5 generated at the emitter the  
 6 going spike at  $V_1$  & -ve going  
 7 spike at  $V_2$  the period of  
 8 oscillation is given by.

$$T = 2.303 RC \log\left(\frac{1}{1-\eta}\right)$$

$$F = \frac{1}{T}$$

Period & frequency of the  
 1 sawtooth wave is independent of  
 2 the supply  $V_{BB}$  & dependent on  
 3 the values of  $R$ ,  $C$  &  $\eta$   
 4 the amplitude of the  
 5 sawtooth wave is dependent on  
 6 the supply &  $\eta$ . It is  
 7 independent of  $R$  &  $C$  values.

If you have

S

ge that means you are a complete package.



17

WEDNESDAY • AUGUST • 2016

- ① The  $\eta$  value for a VJT is found to be 0.6 if enter base resistance is  $10k\Omega$ , find  $R_{B_1}$  &  $R_{B_2}$

$$R_{BB} = 10k\Omega$$

$$\eta = 0.6$$

$$\eta = \frac{R_{B_1}}{R_{B_1} + R_{B_2}}$$

$$0.6 = \frac{R_{B_1}}{10k\Omega}$$

$$R_{BB} = R_{B_1} + R_{B_2}$$

$$10k\Omega = 6k\Omega + 4k\Omega$$

- ② A VJT has 10V betn its bases if  $\eta = 0.65$ , find stand-off voltage & peak voltage for

$$V_P = \eta V_{BB} + 0.7$$

$$= 0.65 \times 10 + 0.7$$

$$= 6.5 + 0.7$$

$$V_P = 7.2$$

In Aa VJT  $\eta = 0.8$ ,  $V_P = 10 \frac{3}{8} V$

$R_{B_2} = 5k\Omega$  find supply voltage &  $R_B$



Successful people use and give positive energy.

SEPTEMBER 2016

WK 34 (231-135)

M	T	W	T	F	S	S
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30		

2016 • AUGUST • THURSDAY

18

$$V_P = \eta V_{BB} + 0.7$$

$$10.8 = 0.8 \times V_{BB} + 0.7$$

$$9.6 = V_{BB}$$

0.8

$$V_{BB} = 12V$$

$$\eta = \frac{R_{B1}}{R_{BB}}$$

$$0.8(R_{B1} + R_{B2}) = R_{B1}$$

$$0.8 R_{B1} + 5 \times 0.8 = 5$$

$$0.8 R_{B1} = 5 - 4$$

$$R_{B1} = \frac{1}{0.8}$$

$$0.8 R_{B1} + 5 \times 0.8 = R_{B1}$$

$$0.2 R_{B1} = 4$$

$$R_{B1} = \frac{4}{2}$$

$$R_{B1} = 20k \Omega$$

You can't lean a direct ladder to the final, you have to clear the previous terms.



10

FRIDAY • AUGUST • 2016

JULY 2016

S	M	T	W	T	F	S
31				1	2	
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

③ For a sawtooth generator find frequency of oscillation if  $R = 50\text{ k}\Omega$ ,  $C = 0.1\text{ }\mu\text{F}$  &  $n = 0.6$

$$T = 2.303 \text{ RC} \log\left(\frac{1}{1-n}\right)$$

$$= 2.303 \times 50 \times 10^3 \times 0.1 \times 10^{-6} \log\left(\frac{1}{0.4}\right)$$

$$\approx 2.303 \times 50 \times 10^3 \times 0.1 \times 10^{-6} \log\left(\frac{10}{9}\right)$$

$$\begin{aligned} \log 10 &= \log 4 \\ &= 1.0000 - 0.6022 \\ &= 0.3979 \end{aligned}$$

$$= 2.303 \times 50 \times 0.1 \times 10^{-3} \times 0.3979 \text{ sec}$$

$$= 2.303 \times 50 \times 0.3979 \times 10^{-4} \text{ sec}$$

$$= 45.818185 \times 10^{-4} \text{ sec}$$

$$= 48.92 \times 10^{-5} \text{ sec}$$

$$= 45.92 \times 10^{-4} \text{ sec}$$

$$= 4.582 \times 10^{-3} \text{ sec}$$

$$= 4.582 \text{ msec}$$

$$f = \frac{1}{T} = \frac{1}{4.582 \text{ msec}} = 218 \text{ Hz}$$

