

M	T	W	T	F	S	S
30	31				1	
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

2016 • APRIL • THURSDAY

14

## Paper - 2

## BJT (Bipolar Junction Transistor)

8 d BJT or Bipolar Junction  
 9 transistor is a well known bipolar device 9 = e- current conduction  
 10 is due to both the types of charge carriers, holes, and free  $e^-$ .  
 11 If is a semiconducting device formed by sandwiching a thin  
 12 slice of P-Type material between two slices of N type  
 1 material or then slice of  
 2 N type material between 2  
 3 slices of P-type material.  
 4 Accordingly there are  
 5 2 types of transistors NPN and  
 6 PNPN both these transistors  
 7 have 3 separate regions namely  
 8 Emitter Emitter, base and  
 9 Collector. The function of the  
 10 emitter is to emit or inject  
 11 majority carriers into the base  
 12 it is a heavily doped region.



Stand as a basket in life that the obstacles in the form of ball comes and passes away but can't stay permanently.

15


FRIDAY • APRIL • 2016

S	M	T	W	T	F	S
	1	2	3	4	5	
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

ie. there are a large no. of ma. majority carriers in the region, the base has the function of passing the majority carriers coming from the emitter onto the collector. It is therefore a very thin region and lightly doped, i.e. very few majority carriers are present in base.

The collector has the function of collecting the majority carriers coming from the emitter thru. the base. hence it is more wider than the emitter, and also moderately doped.

### Structure

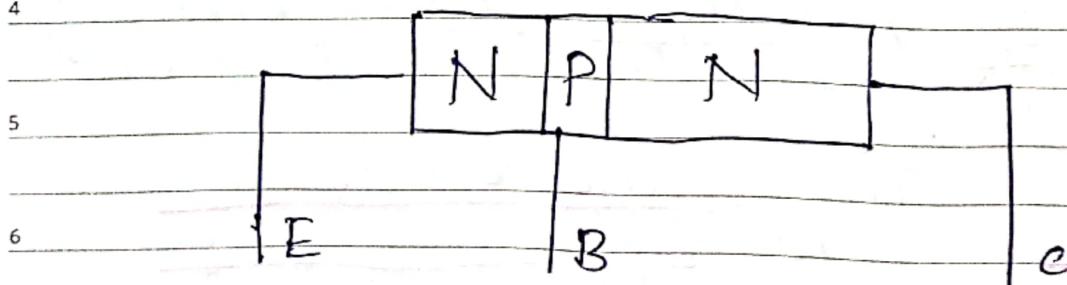


MAY 2016

M	T	W	T	F	S	S
30	31		1			
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

WK 16 (107-259)


2016 • APRIL • SATURDAY

16

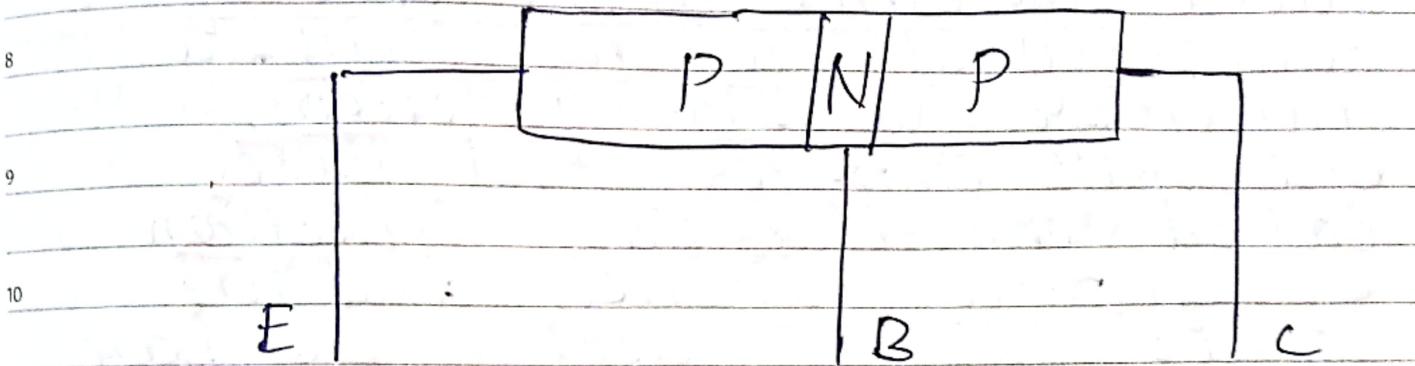

Ej / Cj / FB RB RB Saturation cut off

Symbol

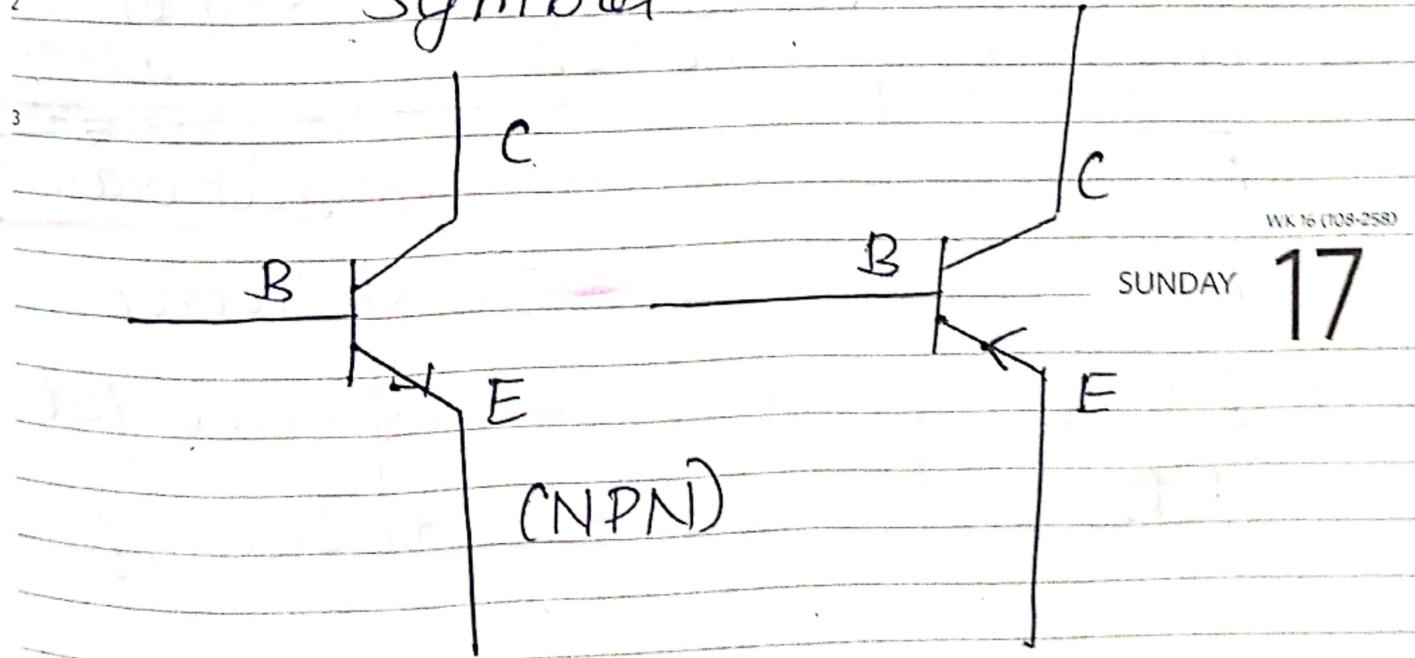

WK 16 (108-258)

SUNDAY

17

Our life is a round trip around achievements, obstacles and actions.



18

MONDAY • APRIL • 2016

S	M	T	W	T	F	S
			1	2	3	4
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

The arrow in the symbol always points in the direction of conventional current flow, a transistor has 2 PN junctions, one betw emitter and base called emitter-base junction or emitter junction and the other betw collector and base called collector-base junction or simply, collector junction. There are four diff. ways of biasing the 2 PN junctions which is shown in the table.

Emitter Junction	Collector Junction	Region of operation
FB	FB →	Saturation
FB	RB →	Active
RB	FB →	Inverted
RB	RB →	Cut-off



Make true relationships, coz fake ones gives nothing except hardships.

MAY 2016

M	T	W	T	F	S	S
30	31	-	-	1	-	-
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

WK 17 (110-256)


2016 • APRIL • TUESDAY

Paper-II

19

# Working of NPN

## transistor

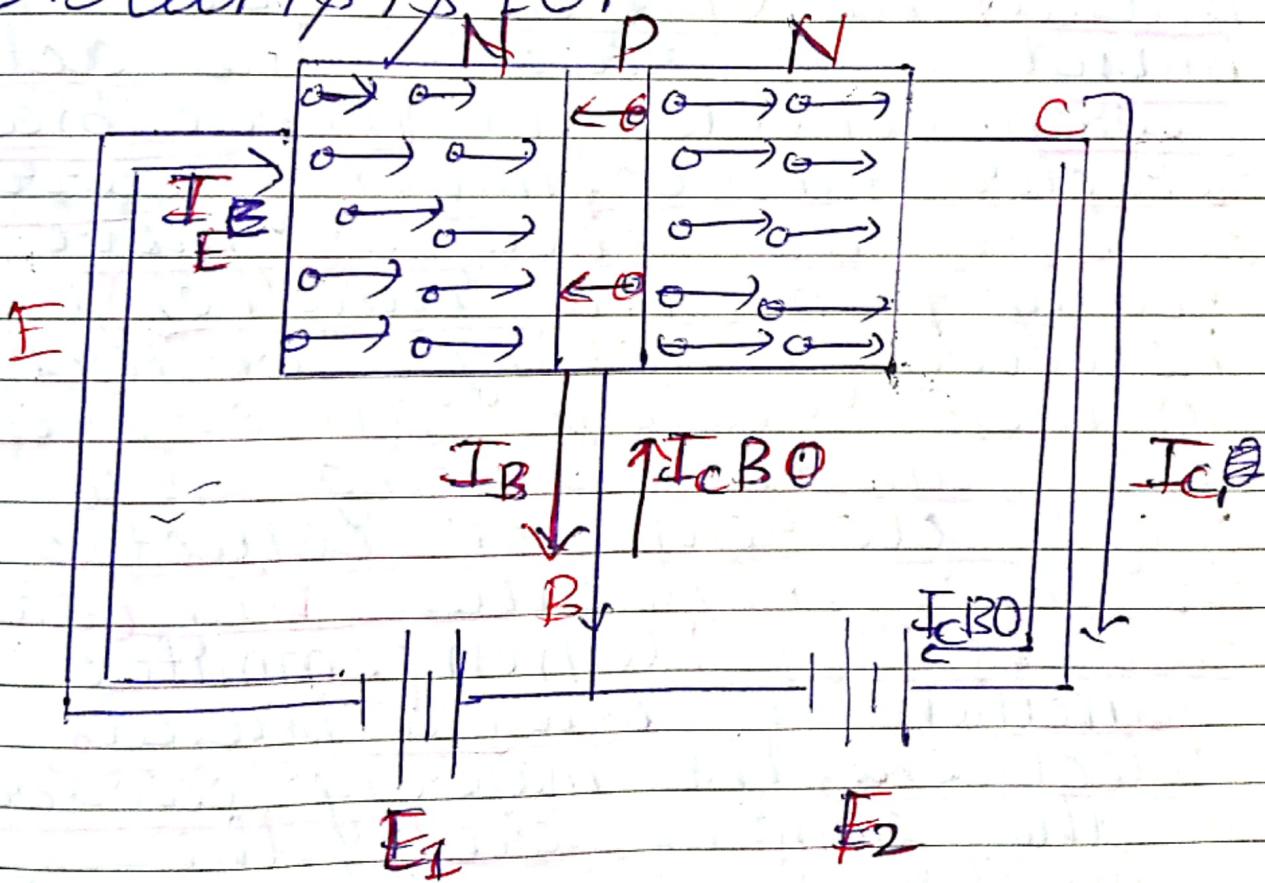

Consider an NPN

Transistor which has  $\text{Q}_{\text{BS}}$  connection made as shown above. Supply  $E_1$  has  $\text{Q}_{\text{BS}}$  +ve terminal connected to

Keep a regular check on your steps that how far you have reached and how long you have to travel for your accomplishment.



20

WEDNESDAY • APRIL • 2016

MARCH 2016

S	M	T	W	T	F	S
	1	2	3	4	5	
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

emitter) and (ve terminal to base.) Emitter junction is forward biased. Collector is made (e) with respect to base by supplying  $E_2$  so that collector junction is reverse biased. The NPN transistor is now biased to operate in the active region. Consider the reverse biased collector junction, majority carriers of base and collector move away from the junction, however, minority carriers in these regions can cross the junction resulting in a small current between collector and base only, called the leakage current  $I_{CBO}$ . When emitter junction is forward biased, electrons, the majority carriers in the emitter cross the emitter junction onto the base, holes in the base cross the junction onto the B emitter. This diffusion of holes and free



MAY 2016

M	T	W	T	F	S	S
30	31		1			
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

WK 17 (II-254)

2016 • APRIL • THURSDAY

21

## Aldwark S. Purao

It is seen because emitter generation is forward biased, recombination occurs near the emitter junction and every recombination eliminates a hole and a free  $e^-$ , however in a transistor emitter is a heavily doped region and base a lightly doped one, the no. of  $e^-$  in the emitter is much more than the no. of holes in the base hence only a few  $e^-$  are lost by the emitter due to recombinations, most of the  $e^-$  from the emitter reach the base and then move on to the collector region, they flow out of the collector towards the +ve terminal of Supply E<sub>2</sub> constituting the current I<sub>C</sub>, at the same time covalent bonds break in the base creating fresh holes and free  $e^-$ , the holes are simply replacing all the



22

FRIDAY • APRIL • 2016

S	M	T	W	T	F	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

holes lost by the base] due to recombination, the  $e^-$  so created flow out of the base constituting a net current  $I_B$ , a large no. of  $e^-$  from base and collector reach the +ve terminal of  $E_I$ . From the -ve terminal  $e^-$  enter the emitter constituting the emitter current  $I_E$ , the flow of  $e^-$  into or out of the collector is called the collector current and here the total collector current has two parts,

- ① Due to  $I_{CBO}$
- ② Due to  $I_{C1}$

$$\therefore I_C = I_{C1} + I_{CBO}$$

The total base current of the transistor  $I_B = I_{B1} - I_{CBO}$  and  $I_E = I_C + E I_B$




MAY 2016  
 M T W T F S S  
 30 31 1  
 2 3 4 5 6 7 8  
 9 10 11 12 13 14 15  
 16 17 18 19 20 21 22  
 23 24 25 26 27 28 29

WK 17 (114-252)

2016 • APRIL • SATURDAY

23

## Working of PNP

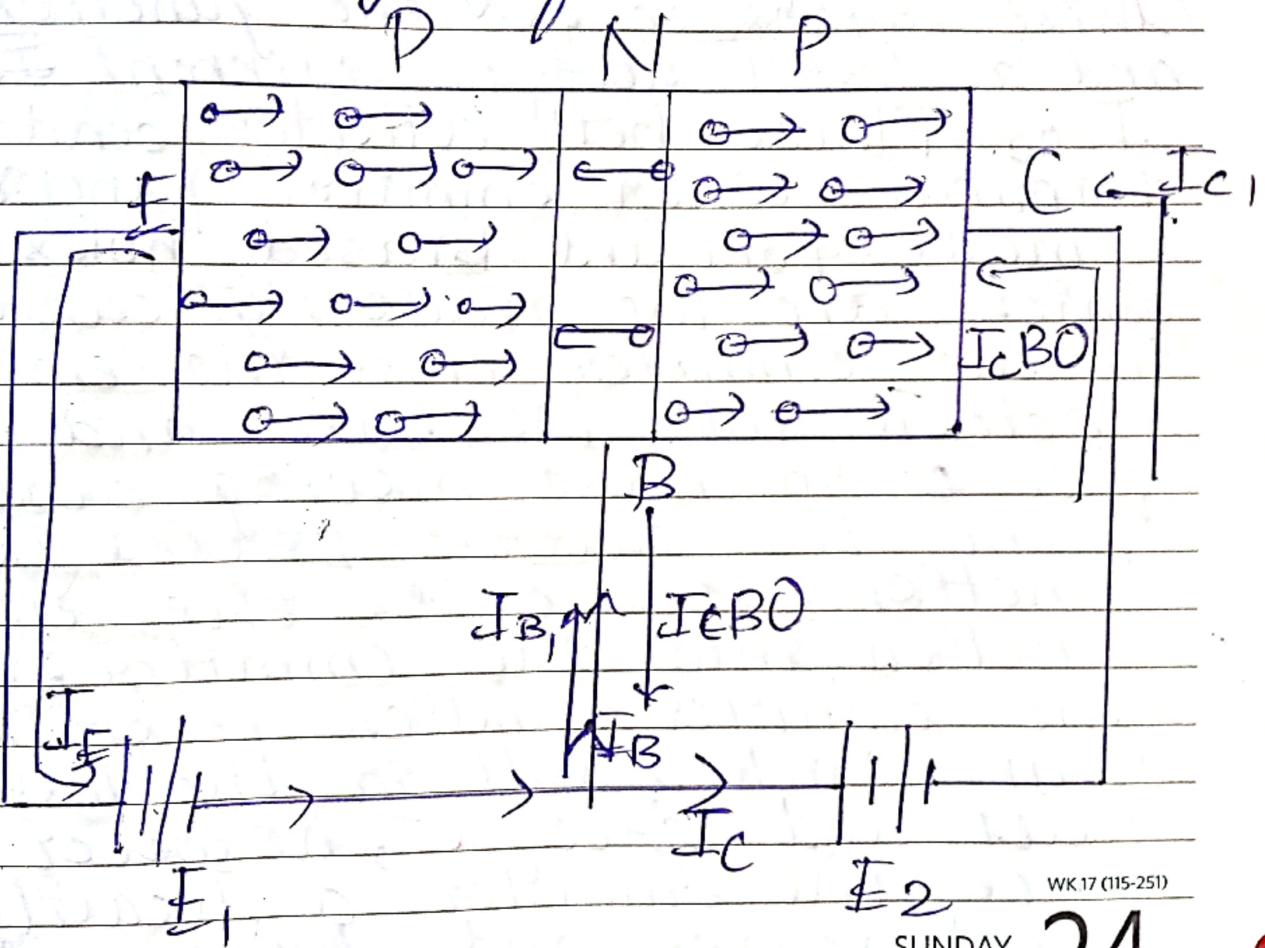

WK 17 (115-251)

SUNDAY

24

Emmilee 98 +ve

went base and collector +ve  
 went base, ∵ the PNP transistor  
 is biased to operate in the active  
 region with collector function reverse

Ladder to future is not ready made,  
 but you have to build it using your tools.



25

MONDAY • APRIL • 2016

MARCH 2016

S	M	T	W	T	F	S
	1	2	3	4	5	
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		


biased, no majority carriers in collector and base can cross the junction, only minority carriers of these regions cross the junction and a small reverse current  $I_{CBO}$  flows between collector and base terminals, when emitter function is made forward biased holes which are the majority carriers in the emitter cross the emitter junction into the base and free  $e^-$  in base moving away from the reverse biased collector junction, now cross the emitter junction into the emitter, near the emitter junction recombinations occur which result in the loss of holes and free  $e^-$ , however since the emitter is a heavily doped region and base a lightly doped one, only a few holes are lost by the emitter due to recombinations, most of the holes reach the collector from the emitter, for every such hole that reaches the collector



A successful team is one when the leader reaches its goal it pulls out other members to grace the achievement.

MAY 2016						
M	T	W	T	F	S	S
30	31		1			
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

WK 18 (117-249)

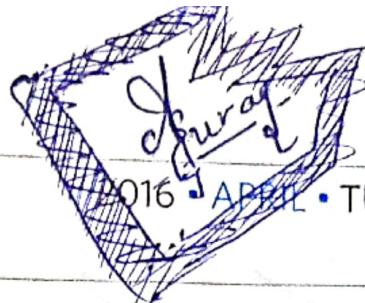

26

an  $e^-$  is released from the -ve terminal of  $E_2$  to neutralize that hole, the flow of  $e^-$  into the collector constitutes the current  $I_{CB}$ , at the same time covalent bonds are broken in the emitter creating fresh holes and free  $e^-$ .

These  $e^-$  flow out of the emitter towards the +ve terminal of  $E_1$ , constituting the emitter current  $I_E$ , from the -ve terminal of  $E_1$ , a few  $e^-$  enter the base to replace those  $e^-$  lost by the base due to recombinations, this constitutes the current  $I_B$ , the total base current is  $98 \text{ } \mu\text{A}$ .

$$I_B = I_B - I_{CBO} \quad I_E = I_C + I_B$$

$$I_C = I_C - I_{CBO}$$

|



27

WEDNESDAY • APRIL • 2016

MARCH 2016						
S	M	T	W	T	F	S
			1	2	3	4
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

19

20

21

22

23

24

25

26

27

28

29

30

31

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

16

17

18

MAY 2016

M	T	W	T	F	S	S
30	31			1		
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29


WK 18 (119-247)

2016 • APRIL • THURSDAY

28

configurations/modes or 3 diff.  
ways of using a transistor as  
an amp/effector

Common base configuration / CB mode

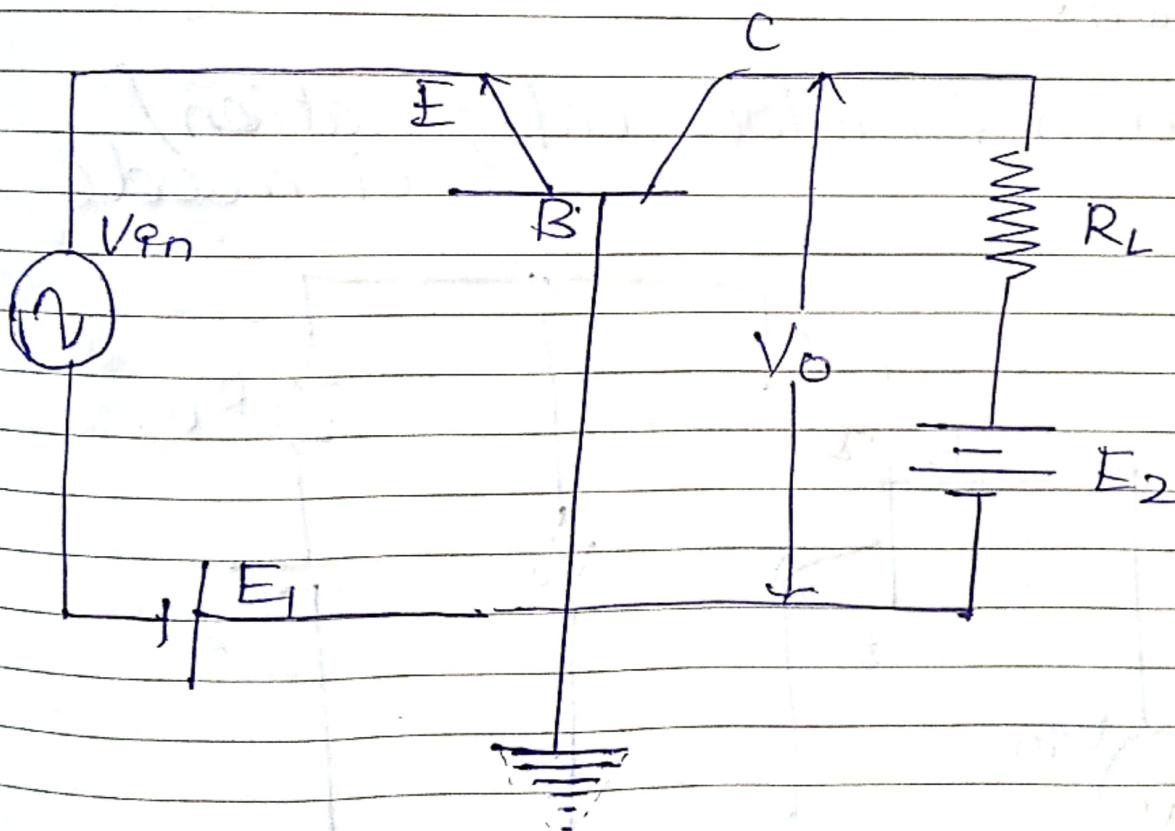

This configuration is  
so called "base is the common  
terminal common to input and




29

FRIDAY • APRIL • 2016

MARCH 2016						
S	M	T	W	T	F	S
			1	2	3	4
6	7	8	9	10	11	5
13	14	15	16	17	18	12
20	21	22	23	24	25	19
27	28	29	30	31		26

output circuits the signal to be amplified  $V_{in}$  is given to the input terminal i.e. emitter, and the amplified output ( $V_o$ ) is obtained at the collector, supplies  $E_1$  and  $E_2$  biased the transistor onto the active region.
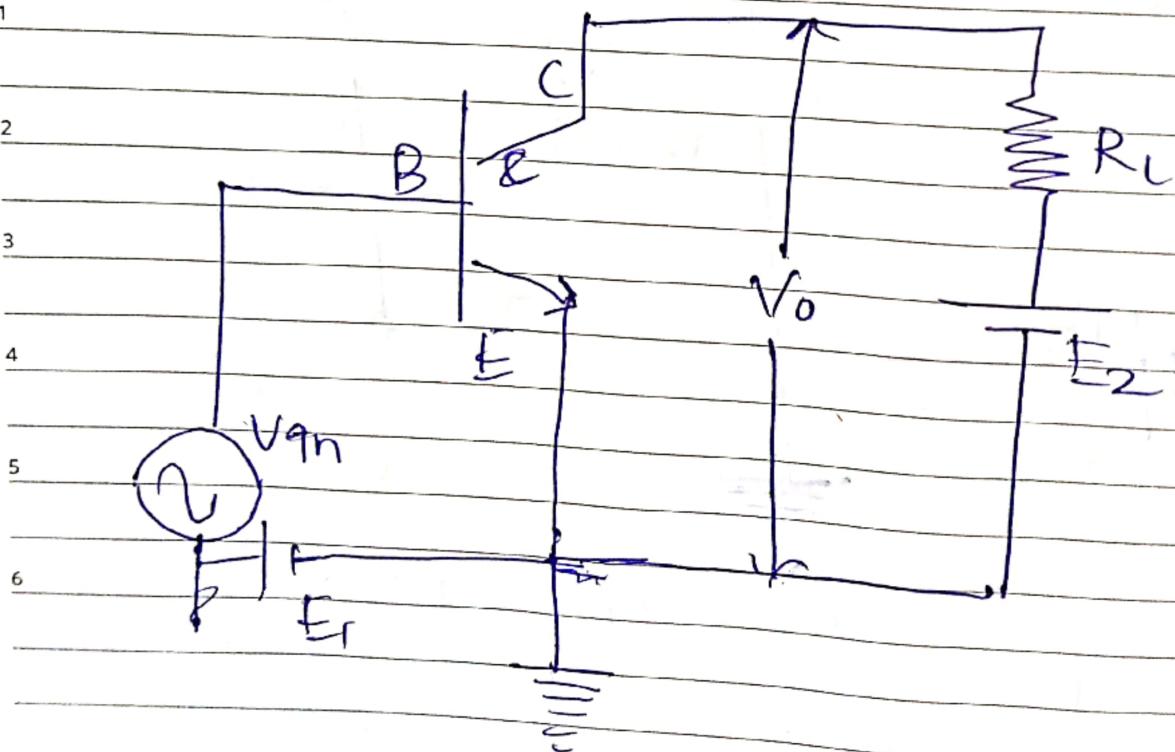
## Common Emitter Configuration / CE mode



A good relationship never leaves you in isolation  
even if you are far a hook of attraction is still hanged.

MAY 2016  
 M T W T F S S  
 30 31 1  
 2 3 4 5 6 7 8  
 9 10 11 12 13 14 15  
 16 17 18 19 20 21 22  
 23 24 25 26 27 28 29


WK 18 (121-245)

2016 • APRIL • SATURDAY

30

In this mode Emitter is the common terminal, base the input terminal and collector output terminal.  $E_1$  and  $E_2$  supplies biased the transistor into the active region.

### CC mode

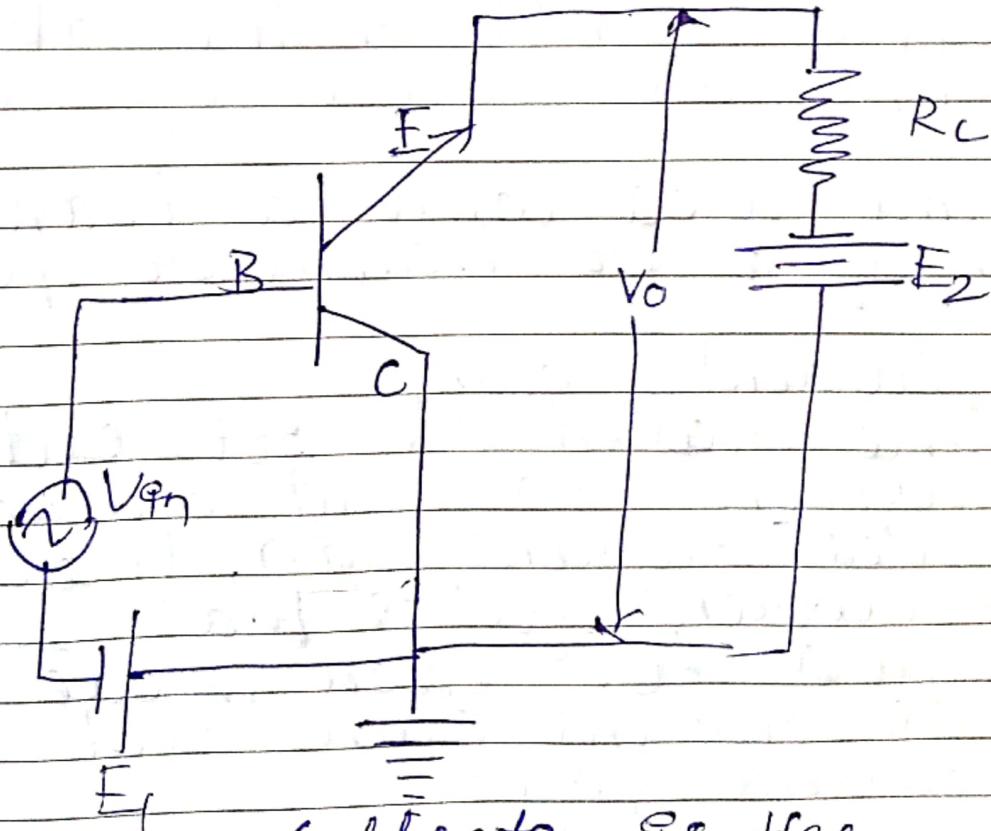

Collector is the





common terminal in the mode, Emitter is the output terminal and base the input terminal supply  $E_1$  reverse biases the collector junction and  $E_2$  forward biases the Emitter junction so that transistor is biased into active region.


Note:

For a PNP transistor all the supply polarities in the above configurations should be reversed.

Terms used with a transistor amplifier or transistor parameters

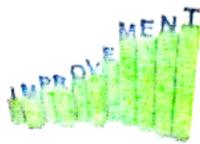(i) current gain

The ratio of net output current to input current is called current gain, there are 2 current gains that can be found for each mode i.e. DC current gain and AC current gain



Improvement is based on your performance,  
more hard you work more you will improve.

S	M	T	W	T	F	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30					

1

SUNDAY • MAY • 2016

8 DC Current gain is the ratio of DC output current to DC input current.

9 AC Current gain is the ratio of change in output current to the change in input current.

11 The current gain in the [CB] mode is indicated by  $\alpha$ .  
 12 For this mode output current is collector current and input current is emitter current.  $\therefore \alpha_{DC}$

$$\alpha_{DC} = \frac{I_C}{I_E}$$

5 where  $I_C$  and  $I_E$  are the DC values of collector and emitter currents respectively.



M	T	W	T	F	S	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30			

2016 • MAY • MONDAY

2

$$\alpha_{AC} = \frac{\Delta I_C}{\Delta I_E}$$

8

$$\alpha_{AC} = \frac{\Delta I_C}{\Delta I_E}$$

10

$\alpha_{AC}$  indicates change in collector current due to a change  $\Delta I_E$  in emitter current. The value of  $\alpha$  is found at a particular collector to base voltage and is always less than 1 because collector current of a transistor is always less than its emitter current. (The current gain in the CE mode is indicated by  $B$ . Base current is the input current and collector current is the output current)

$$\therefore B = \frac{I_C}{I_B}$$

$$B = \frac{I_C}{I_B}$$



3

TUESDAY • MAY • 2016

S	M	T	W	T	F	S
3	4	5	6	7	8	1
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

8

The value of  $\beta$  is found at a particular collector to emitter voltage and it is very high because base current of a transistor is normally  $1 \mu A$ , whereas its collector current is much greater in mA. The current gain in the CC mode is indicated by  $\gamma$

2

3

$$\gamma_{dc} = \frac{\Delta I_C}{\Delta I_B}$$

4

5

$$\gamma_{ac} = \frac{\Delta I_C}{\Delta I_B}$$

6

The value of  $\gamma$  is found at a particular



JUNE 2016

M	T	W	T	F	S	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30			

WK 19 (125-241)

2016 • MAY • WEDNESDAY

4

1 collector emitter voltage and  $\alpha$   
 2 also very high.

3 Relation bet<sup>n</sup>  $\alpha$  and  $\beta$

$$10 \quad \alpha = \frac{I_C}{I_E} = \frac{I_C}{I_C + I_B} = \frac{\beta I_B}{\beta I_B + I_B} = \frac{\beta}{1 + \beta}$$

11 the same relation can  
 12 also be written as

$$1 \quad \beta = \frac{\alpha}{1 - \alpha}$$

$$3 \quad I_E = I_C + I_B$$

4  $\therefore$  divide by  $I_B$

$$5 \quad \frac{I_E}{I_B} = \frac{I_C + I_B}{I_B}$$

$$6 \quad \gamma = \beta + 1$$

A successful team members allow one to stand at the top and are happy to support from the bottom.



5

THURSDAY • MAY • 2016

S	M	T	W	T	F	S
						1
3	4	5	6	7	8	2
10	11	12	13	14	15	9
17	18	19	20	21	22	16
24	25	26	27	28	29	23
						30

# Relation bet<sup>n</sup>

8       $\gamma$  and  $\alpha$

10       $I_E = I_C + I_B$

11       $\therefore$  thrg. by  $I_E$

12       $I = \frac{I_C}{I_E} + \frac{I_B}{I_E}$

1       $I - \alpha = \frac{I_B}{I_E}$        $\therefore \alpha = \frac{I_C}{I_E}$

3       $\therefore \gamma = -\frac{I_E}{I_B} = -\frac{1}{1-\alpha}$

5      Get in a certain  
transistor circuit a change  
in emm. current of  $1 \text{ mA}$   
produces a change in collector  
current of  $0.99 \text{ mA}$ , find  
current gain



No matters if you win or loose you will gain experience with both.

JUNE 2016

M	T	W	T	F	S	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30			

WK 19 (127-239)

2016 • MAY • FRIDAY

6

$$\alpha_{dc} = \frac{\Delta I_C}{\Delta I_E} = \frac{0.99}{1} = 0.99 \text{ mA}$$

If the current gain of the transistor in the CE mode is 100, find  $\alpha$

$$\alpha_{CE} = \beta = 100$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{101} = 0.99$$

③ For a certain transistor  $\alpha_{dc} = 0.98$  and emm. current equals to 2 mA find collector and base current

$$\alpha_{dc} = 0.98$$

$$I_E = 2 \text{ mA}$$

$$I_C, I_B$$

$$\alpha_{DC} = \frac{I_C}{I_E}$$

$$I_C = \alpha_{DC} \times I_E = 1.96 \text{ mA}$$

$$I_E = I_C + I_B$$



Truth and lie are like twin brothers, it is upon you how you will identify.

10

TUESDAY • MAY • 2016

S	M	T	W	T	F	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30					

$$I_B = (2 - 1.96) \text{ mA}$$

$$I_B = 0.04 \text{ mA}$$

9. Q4. Collector current equals 2.9mA  
 for a transistor if base current  
 10. equals to ~~2.9mA~~ for a transistor  
 $100 \mu\text{A}$

11. find  $\alpha$  DC

$$I_C = 2.9 \text{ mA}$$

$$I_B = 100 \mu\text{A}$$

$$\alpha_{DC} = \frac{I_C}{I_E} = \frac{2.9}{3} = 0.96 \text{ mA}$$

3. (5) In a transistor base current is  $68 \mu\text{A}$  emm. current is  $30 \text{ mA}$  &  
 4.  $\beta$  equals to 440. find  $\alpha$  and collector current

$$I_E = I_C + I_B$$

$$30 = I_C + 0.068$$

$$I_C = 30 - 0.068$$

$$I_C = 29.932 \text{ mA}$$



Live a balanced life, work to live and live to work.

JUNE 2016  
 M T W T F S S  
 1 2 3 4 5  
 6 7 8 9 10 11 12  
 13 14 15 16 17 18 19  
 20 21 22 23 24 25 26  
 27 28 29 30

WK 20 (132-234)

2016 • MAY • WEDNESDAY

11

$$\alpha = \frac{\beta}{1+\beta} = \frac{440}{441}$$

⑥ In a CB mode current amplification factor is 0.9, if emm-current equals to  $I_{mA}$  find base current

$$\alpha = 0.9 \quad I_E = I_B + I_C$$

$$\alpha = \frac{I_C}{I_E} : I_B = I_E - I_C \\ = 1 - 0.9 \\ = 0.1 \text{ mA}$$

$$0.9 = \frac{I_C}{1 \times 10^{-3}}$$

$$I = 0.9 \text{ mA}$$

⑦ From the table given below find the current gain in the CB mode

$V_{CE}$ (V)	$I_C$ mA $I_B = 25 \mu\text{A}$	$I_B = 65 \mu\text{A}$
5V	0.91	2.25
5V	0.92	2.45



12

THURSDAY • MAY • 2016

APRIL 2016

S	M	T	W	T	F	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

B1

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$= \frac{2.25 - 0.9}{65 - 25}$$

$$= \frac{1.34 \text{ mA}}{40 \mu\text{A}}$$

$$\beta_{AC} = 33.5$$

$$\begin{array}{r} 6.95 \\ - 0.92 \\ \hline 1.53 \end{array}$$

$$\beta_{AC} = \frac{\Delta I_C}{\Delta I_B} = \frac{2.45 - 0.92}{65 - 25} = \frac{1.53}{40}$$

$$= \frac{1.53 \text{ mA}}{40 \mu\text{A}}$$

$$= \frac{1.53 \times 10^{-3}}{40} \times 10^3$$

$$= 0.03825 \times 10^3$$

$$= 38.25$$

Q8. In a CB mode  $\alpha$  equals to 0.95 and voltage drop across 2K $\Omega$  resistor which is

**SOLUTION**


A solution is generated before any problem arises  
but it remains incognito coz we focus more on problems.

JUNE 2016

M	T	W	T	F	S	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30			

WK 20 (134-232)

2016 • MAY • FRIDAY

13

connected to the collector is 2V  
 find base current.

$$I_C R_L = V_{RL}$$

$$I = \frac{V_{RL}}{R_L}$$

$$= \frac{2}{2 \times 10^3} \\ = 10^{-3}$$

$$I_C = 1 \text{ mA}$$

$$I_E = \frac{I_C}{\alpha}$$

$$= \frac{1}{0.95}$$

$$I_E = 1.05 \text{ mA}$$

$$I_B = I_E - I_C \\ = 1.05 - 1 \\ = 0.05 \text{ mA}$$



Don't run after those who are in heights,  
 rather design your own craft to fly even with higher speed.

14

SATURDAY • MAY • 2016

APRIL 2016

S	M	T	W	T	F	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Q.9 For a CE transistor

 $\beta = 45$  and voltage drop across8.  $1\text{ k}\Omega$  resistor which is connected in the collector.9. circuit is  $11\text{V}$ . Find  $I_B$ 

$$I_C = 1\text{mA}, \beta = 45$$

10.

$$\beta = \frac{I_C}{I_B}$$

11.

$$I_B = \frac{1}{45}$$

12.

$$I_B = 0.022$$

13.

 $\Rightarrow$  Q1 Input resistance

15 SUNDAY The resistance offered by a resistor betn its input terminals is called Input resistance. Suppose points 1 & 2 indicate the terminals  $R_i$ ,  $V_s$  a voltage extended from external source and  $R_s$  internal resistance of a voltage source.



JUNE 2016


M	T	W	T	F	S	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30			

Today -

WK 21 (137-229)

2016 • MAY • MONDAY

16

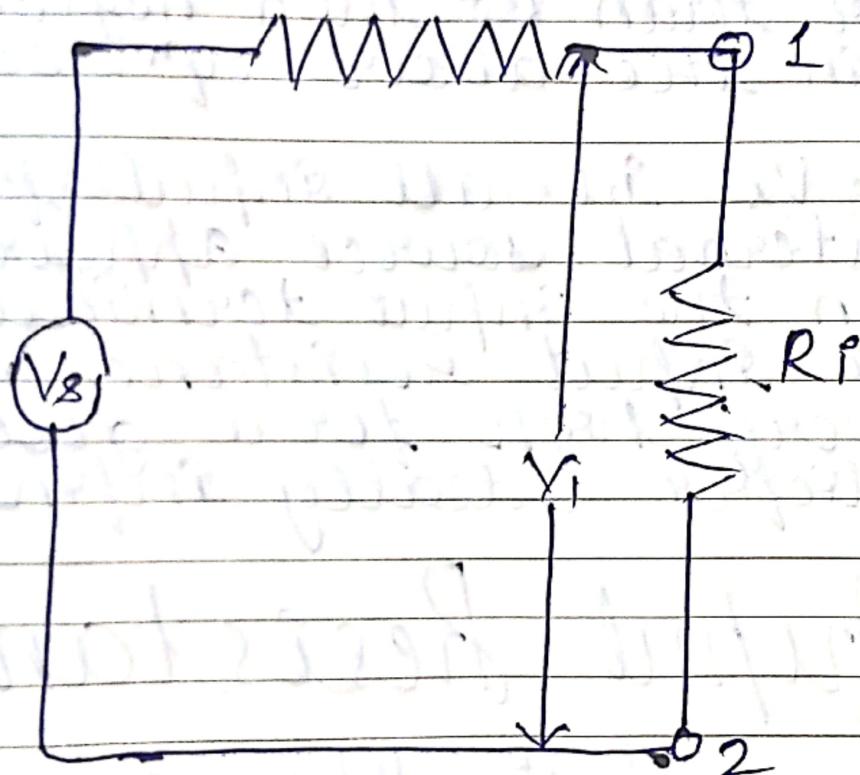

The actual input to the amplifier  
P. e.: voltage across  $R_p$  in the  
above figure is given by

$$V_i = IR_1$$

$$= \left( \frac{V_s}{R_s + R_1} \right) R_1$$

$$V_i = \frac{R_1}{R_s + R_1} \times V_s$$



17

TUESDAY • MAY • 2016

S	M	T	W	T	F	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

If  $R_i$  is very much greater than  $R_s$  then neglecting  $R_s$  in the "above eq" we have,

$V_i = V_o$  i.e. all input from the external source appears between the input terminals. hence Input resistance must be very high for a good amplifier ideally infinite.

## ⇒ Output Resistance

Just like a voltage source an amplifier also has some internal resistance which is called its output resistance  $R_o$  ( $R_{zero}$ ). In the figure shown below points 3 & 4 indicate the output terminals of the amplifier.

$V_o$  ( $V_{zero}$ ) is the output voltage and  $V_L$  is the actual voltage delivered to the load  $R_L$ .



Quality of leadership is among all of us, all we need to work hard.

JUNE 2016


M	T	W	T	F	S	S
1	2	3	4	5		
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30			

WK 21 (139-227)

2016 • MAY • WEDNESDAY

18

3

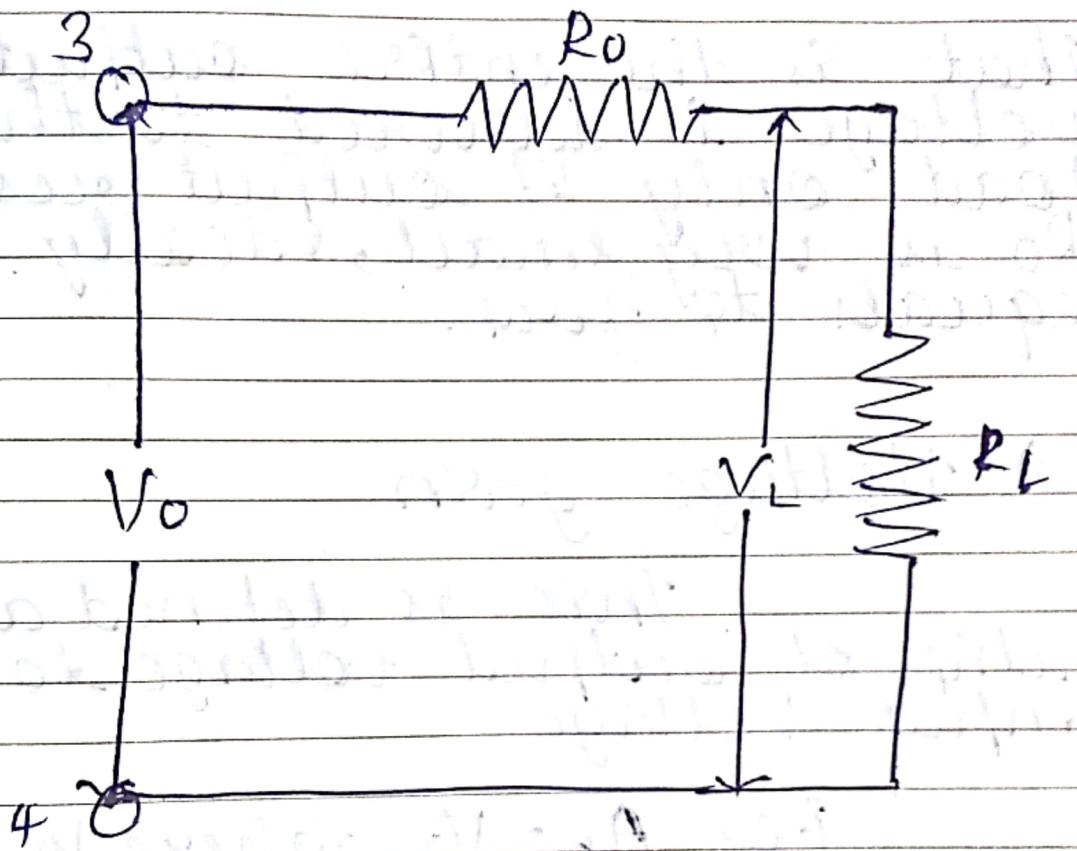

$$V_L = I \times R_2$$

$$= \frac{V_o}{R_o + R_L} \times R_L$$

$$V_L = \left( \frac{R_L}{R_o + R_L} \right) V_o$$

If  $R_o$  is very much less than  $R_L$  then  $V_L = V_o$ .



19

THURSDAY • MAY • 2016

S	M	T	W	T	F	S
					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

That is the entire output voltage is delivered to the load only if output resistance  $R_o$  is very small, ideally equals to zero.

=) Voltage gain

This is defined as the ratio of output voltage to input voltage

i.e.  $A_v = \frac{V_o}{V_i}$  where  $V_o$  is

the input voltage and  $V_o$  is the output of the amplifier.

4

5

6

